

ECE 145b Homework #2 Solutions

#1

$$\sigma_x = 2 \text{ mV}$$

Error if $+10 \text{ mV}$ received and $V_{\text{noise}} \leq -10 \text{ mV}$
or
 -10 mV received and $V_{\text{noise}} \geq 10 \text{ mV}$

$$P[X \geq 10 \text{ mV}] = P[X \leq -10 \text{ mV}] = 1 - \Phi\left(\frac{x - \mu}{\sigma_x}\right) = 1 - \Phi\left(\frac{10 - 0}{2}\right) = Q(5)$$

from statistics: $Q(5) \approx 2.86 \times 10^{-7}$
for either $\pm 10 \text{ mV}$,

$$\underline{P_{\text{error}} = 2.86 \times 10^{-7}}$$

#2

$$\tilde{S}_{v_{in}v_{in}} = 4kTR_0FG$$

$$R_0 = 50 \Omega, F = 2, G = 10^5, \text{ assume } T = 300 \text{ K}$$

$$\tilde{S}_{v_{in}v_{in}} = 1.66 \times 10^{-13} \text{ V}^2/\text{Hz}$$

$$a) V_{out1}(j\omega) = h_1(j\omega) V_{in}(j\omega)$$

$$\tilde{S}_{v_{out1}v_{out2}} = |h_1(j\omega)|^2 \tilde{S}_{v_{in}v_{in}}$$

$$\tilde{S}_{v_{out1}v_{out2}} = h_1(j\omega) h_1^*(j\omega) \tilde{S}_{v_{in}v_{in}}$$

$$= \left(\frac{1}{1 + j\frac{f}{f_0}} \right) \left(\frac{1}{1 - j\frac{f}{f_0}} \right) \tilde{S}_{v_{in}v_{in}}$$

$$\underline{\tilde{S}_{v_{out1}v_{out1}} = \frac{\tilde{S}_{v_{in}v_{in}}}{1 + \left(\frac{f}{f_0}\right)^2}}$$

similarly,

$$\underline{\tilde{S}_{v_{out2}v_{out2}} = \frac{\tilde{S}_{v_{in}v_{in}}}{1 + \left(\frac{f}{f_0}\right)^2}}$$

$$\tilde{S}_{v_{out1}v_{out2}} = V_{out1}(j\omega) V_{out2}^*(j\omega) = h_1(j\omega) V_{in}(j\omega) h_2^*(j\omega) V_{in}^*(j\omega)$$

$$b) \tilde{S}_{v_{out3}v_{out3}} = (V_{out1} + V_{out2})(V_{out1}^* + V_{out2}^*)$$

$$= \tilde{S}_{v_{out1}v_{out1}} + \tilde{S}_{v_{out2}v_{out2}} + 2 \text{Re}[\tilde{S}_{v_{out1}v_{out2}}]$$

$$\underline{\tilde{S}_{v_{out1}v_{out2}} = \frac{\tilde{S}_{v_{in}v_{in}}}{(1 + j\frac{f}{f_0})(1 - j\frac{f}{f_0})}}$$

$$\tilde{S}_{v_{out3}v_{out3}} = \left[\frac{1}{1 + \frac{f}{f_0}} + \frac{1}{1 + \frac{f}{f_0}} + 2 \frac{1 + \frac{f}{f_0} \frac{f}{f_0}}{(1 + \frac{f}{f_0})(1 + \frac{f}{f_0})} \right] \times \tilde{S}_{v_{in}v_{in}}$$

#3

$$S_{w, \text{noise}} = 4KTR \quad R_{\text{gen}} = 100\Omega$$

$$S_{w, \text{noise}} = 1.66 \times 10^{-18} \text{ V}^2/\text{Hz} = 1.66 \times 10^{-18} \text{ V}^2 \text{ in } 1\text{Hz BW}$$

$$\frac{S}{N} = \frac{|V_{\text{gen}}|^2 (V^2)}{|V_{\text{noise}}|^2 (V^2)} = \frac{(1\text{V})^2}{(1.66 \times 10^{-18} \text{ V}^2)} = 6.04 \times 10^{17} = \underline{177.8\text{dB}}$$



$V_{\text{noise, rms}} = \sqrt{S_{w, \text{noise}}}$, signal should be left in RMS as well

#4

$$\tilde{S}_{\text{in, via}} = 4KTR_{\text{via}} F_6 = 1.66 \times 10^{-18} \text{ V}^2/\text{Hz} \quad @ T = 300\text{K}$$

$$\tilde{S}_{\text{vco, out}} = \|h(j\omega)\|^2 \tilde{S}_{\text{in, via}} = \frac{1.66 \times 10^{-18} \text{ V}^2/\text{Hz}}{1 + \left(\frac{f}{161\text{Hz}}\right)^2}$$

#5

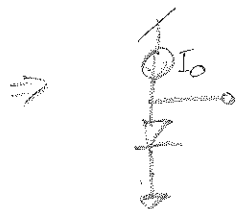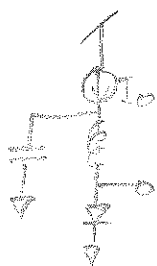

$$V_{\text{diode}} = \frac{KT}{qI_0}$$




$$\frac{d\langle E_{\text{diode}}, E_{\text{diode}} \rangle}{dt} = \frac{d\langle E_{\text{diode}}, E_{\text{diode}} \rangle}{dt} \cdot r_{\text{diode}} = \frac{2KT^2}{qI_0}$$

$$\frac{dP_{\text{diode}}}{dt} \frac{d\langle E_{\text{diode}}, E_{\text{diode}} \rangle}{4P_{\text{diode}}} = \frac{KT}{2} [J]$$

Noise is $1/2$ what's expected for resistor of same impedance.
Due to 1-way current flow

#6

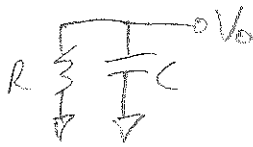

$$Z = R \parallel \frac{1}{sC} = \frac{R}{1 + sRC} = \frac{R}{1 + j2\pi fRC}$$

$$\text{Re}(Z) = \frac{R}{1 + 4\pi^2 f^2 R^2 C^2}$$

$$\frac{d\langle E_n, E_n^* \rangle}{df} = 4kT \text{Re}(Z) = \frac{4kTR}{1 + 4\pi^2 f^2 R^2 C^2} \left(\frac{V^2}{f^2} \right)$$

$$|E_n|^2 = \int_0^\infty \frac{4kTR}{1 + 4\pi^2 f^2 R^2 C^2} df$$

$$|E_n|^2 = \frac{4kTR}{2\sqrt{4\pi^2 R^2 C^2}} = \frac{kT}{C}$$

$$V_0 = \sqrt{\frac{kT}{C}}$$

or from notes:

$$\langle E \rangle = \frac{kT}{2}$$

$$\langle E \rangle = \frac{1}{2} CV^2$$

$$\frac{kT}{2} = \frac{CV^2}{2} \quad V_0 = \sqrt{\frac{kT}{C}}$$