

# ECE 145b Homework #4 Solutions

#1

a)  $f_{IF} + f_{RF} = f_{LO} = 98.7 \text{ MHz}$

$$f_{LO} + f_{IF} = f_{image} = 109.4 \text{ MHz}$$

b)  $f_{LO} = 118.7 \text{ MHz}$

$$f_{image} = 129.4 \text{ MHz}$$


c) Yes,  $f_{IF,min} > f_{RF,max}$ . Needs a step BPF for 88-108 MHz.

#2

$f_1 = 99.8 \text{ MHz}$

a)  $f_2 = 99.6 \text{ MHz}$   $2f_1 - f_2 = 100 \text{ MHz} = f_{RF}$

*hard to see on problem set*  
 $|IP3 = -15 \text{ dBm}$

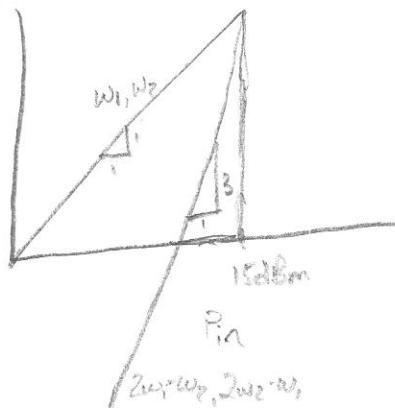

$w_1, w_2$	$2w_1 - w_2, 2w_2 - w_1$
-15 dBm	-15 dBm
-16 dBm	-18 dBm
-17 dBm	-21 dBm
:	
-30 dBm	-60 dBm

$$P_{int} = -60 \text{ dBm} \quad SNR = \frac{P_{sig}}{P_{int}} = 20 \text{ dB} \Rightarrow P_{sig} = \underline{-40 \text{ dBm}}$$

b) For  $P_{sig} = -40 \text{ dBm}$  &  $P_{noise} = 115 \text{ dBm}$ ,  $SNR = 95 \text{ dB}$ , much higher

or  $P_{sig} = -115 \text{ dBm}$  for required  $SNR = 20 \text{ dB}$

#3

$$I = I_s e^{-\frac{eV_{AC}}{kT}}$$

$$V_{AC} = V_0 + \delta V_{in}$$

$$V_{AC} = V_0 \cos(\omega_1 t) + V_0 \cos(\omega_2 t)$$

$$I = I_s e^{-\frac{eV_0}{kT}} \cdot e^{-\frac{\delta V_{in}}{kT}}$$

$$= I_{DC} e^{-\frac{\delta V_{in}}{kT}}$$

$$\approx I_{DC} \left[ 1 + \left( \frac{\delta V_{in}}{V_F} \right) + \frac{1}{2!} \left( \frac{\delta V_{in}}{V_F} \right)^2 + \frac{1}{3!} \left( \frac{\delta V_{in}}{V_F} \right)^3 + \dots \right]$$

$$I_{DC} + I_{AC} =$$

$$\delta V_{in} = \frac{V_0}{2} \left( (z_1 + z_1^{-1}) (z_2 + z_2^{-1}) \right)$$

from notes

$$\left( \delta V_{in} \right)^3 = \frac{V_0^3}{8} \left( 15 \cos(\omega_1 t) + 15 \cos(\omega_2 t) + 2 \cos(3\omega_1 t) + 2 \cos(3\omega_2 t) \right. \\ \left. + 6 \cos(2\omega_1 + \omega_2)t) + 6 \cos(2\omega_2 + \omega_1)t) \right. \\ \left. + 6 \cos((2\omega_1 - \omega_2)t) + 6 \cos((2\omega_2 - \omega_1)t) \right)$$

↑  
what we're concerned with

$$3^{rd} \text{ order int.} \approx \frac{\delta V_{in}}{V_F} \cdot \frac{1}{3!} \left( \frac{\delta V_{in}}{V_F} \right)^3$$

$$\cancel{\frac{V_0}{2} \left[ \cos(\omega_1 t) + \cos(\omega_2 t) \right]} = \frac{V_0^3}{8V_F^2} \cancel{\left[ \cos((2\omega_1 - \omega_2)t) + \cos((2\omega_2 - \omega_1)t) \right]} \\ \cancel{\times V_F^3}$$

$$I = \frac{V_0^2}{8V_F^2} \quad V_F = 2\sqrt{2} V \approx \underline{73.5 mV}$$

$$I_{AC} = g_m V_{AC}$$

$$I_{AC} = \frac{I_C}{V_F} \cdot (2\sqrt{2} V) = 2\sqrt{2} (1mA) \approx \underline{2.83 mA}$$

$$g_m = \frac{I_C}{V_F}$$

#4

$$I_d = K(V_{gs} - V_{th})^2 \quad K: 10mA/V^2 \quad V_{th} = 0.3V$$

$$I_d = 3mA$$

$$(V_{gsdc} - 0.3V) = \sqrt{\frac{3mA}{10mA/V^2}}$$

$$V_{gsdc} = 0.848V$$

$$I_{AC} + I_{DC} = K(V_{gsdc} + V_{AC} - V_{th})^2$$

$$I_{AC} + 3mA = K(V_{AC} + V_{DC})^2$$

$$V_{gsdc} - V_{th} = V_{AC}$$

$$I_{AC} + 3mA = K(V_{AC}^2 + 2V_{AC}V_{DC} + V_{DC}^2)$$

from notes:

$$I_{AC} = K\left(\frac{16}{2}\right)^2 [2 + 2\cos(2\omega_1 t) + 2\cos(2\omega_2 t) + 4\cos(2(\omega_1 + \omega_2)t) + 4\cos(2(\omega_1 - \omega_2)t)] \\ + K \cdot 2 \cdot V_0 \cdot V_{AC} [\cos(\omega_1 t) + \cos(\omega_2 t)]$$

$$\text{additional DC} = 5nA$$

$$\pm \omega_1 / \omega_2 = 10.96\mu A$$

$$\pm 2\omega_1 / 2\omega_2 = 5nA$$

$$\pm 2(\omega_1 + \omega_2) / 2(\omega_1 - \omega_2) = 10nA$$