

EECE 2C Problem Set #2 Solution

#1

For Mobility Limited FET

$$I_d = \left(\frac{\mu C_{ox} W_g}{2 L_g} \right) (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$\frac{\mu C_{ox} W_g}{2 L_g} = 1 \text{ mA/V}^2, \quad V_{th} = 0.3 \text{ V}, \quad \lambda = 0.1 \text{ V}^{-1} \text{ \& Given!}$$

(a)

$$V_{ds} = 2 \text{ V} \quad \& \quad I_d = 0.5 \text{ mA}$$

$$\Rightarrow 0.5 \text{ mA} = \overset{\substack{\uparrow \\ \text{DC bias}}}{1 \text{ mA/V}^2} \cdot \overset{\substack{\uparrow \\ \text{Drain Current!}}}{(V_{gs} - 0.3 \text{ V})^2} (1 + 0.1 \text{ V}^{-1} \cdot 2 \text{ V}) \text{ \& } I_d$$

$$\Rightarrow V_{gs} = \sqrt{\frac{0.5}{1.2}} + 0.3 = \underline{0.945 \text{ V}}$$

Transconductance


$$\Rightarrow g_m = \frac{2 I_D}{2 V_{gs}} = \left(\frac{\mu C_{ox} W_g}{L_g} \right) (V_{gs} - V_{th}) (1 + \lambda V_{ds})$$

$$= 2 \text{ mA/V}^2 \cdot (0.945 - 0.3) (1 + 0.2) = \underline{1.548 \text{ mA/V}}$$

Output Conductance

$$G_{ds} = \frac{2 I_D}{2 V_{ds}} = \frac{\lambda I_D}{1 + \lambda V_{ds}} = \frac{0.1 \text{ V}^{-1} \times 0.5 \text{ mA}}{1 + 0.2} = \underline{0.416 \text{ mA/V}}$$

(b) (Small signal circuit)

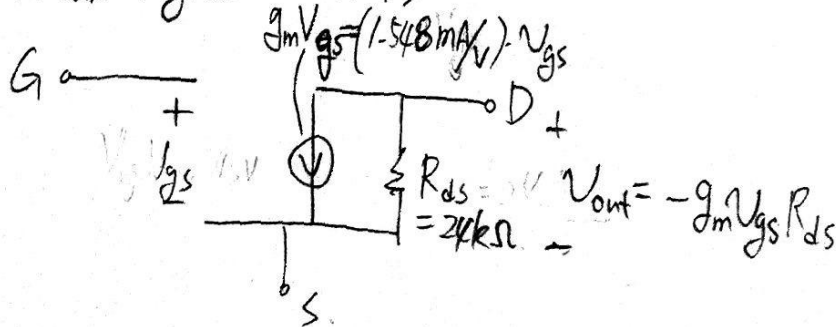

$$= \frac{1}{R_{ds}} \Rightarrow R_{ds} = \underline{2 \text{ k}\Omega}$$

$$\frac{\text{V}}{\text{mA}} = 10^3 \frac{\text{V}}{\text{A}}$$

#2.

For Velocity limited FET

$$I_d = V_{sat} C_{ox} W_g (V_{gs} - V_{th}) (1 + \lambda V_{ds}) \quad \& \text{ Current equation}$$

$$V_{sat} C_{ox} W_g = 0.5 \text{ mA/V}, \quad \lambda = 0.1 \text{ V}^{-1}, \quad V_{th} = 0.3 \text{ V} \quad \& \text{ given}$$

(a)

$$V_{ds} = 1 \text{ V}, \quad V_{gs} = 0.5 \text{ V}$$

Transconductance

$$\Rightarrow g_m = \frac{\partial I_d}{\partial V_{gs}} = \frac{C_{ox} V_{sat} W_g}{0.5 \text{ mA/V}} (1 + \lambda V_{ds}) = \frac{0.55 \text{ mA/V}}{0.1 \text{ V}^{-1} \cdot 1 \text{ V}}$$


to get G_{ds} , we need I_d value first,


$$I_d = 0.5 \text{ mA/V} \cdot (0.5 \text{ V} - 0.3 \text{ V}) (1 + 0.1) = \underline{0.11 \text{ mA}}$$

Output Conductance

$$\Rightarrow G_{ds} = \frac{\partial I_D}{\partial V_{ds}} \left(= \frac{1}{R_{ds}} \right) = \frac{0.1 \text{ V}^{-1} \cdot 0.11 \text{ mA}}{1} = \underline{0.011 \text{ mA/V}}$$

(b)

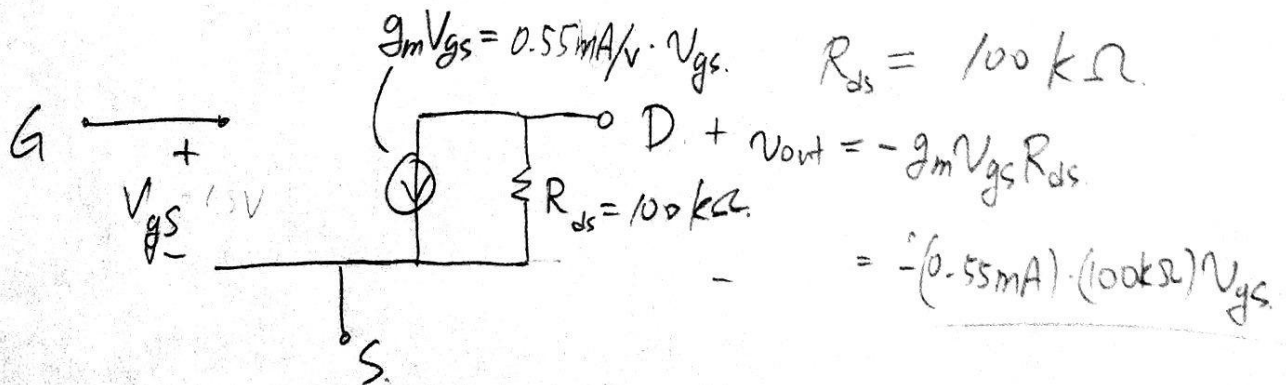

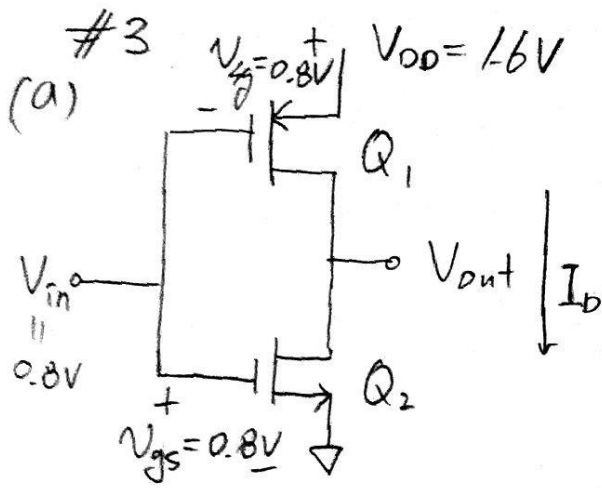

Given Values

L_g	45nm	45nm
t_{ox}	0.8nm	0.8nm
λ	$0.3V^{-1}$	$0.3V^{-1}$
V_{sat}	10^7 cm/s	$0.5 \times 10^7 \text{ cm/s}$
W_g	5 μm	10 μm
V_{th}	0.4V	-0.4V

(b) For DC biasing,

$$I_{D,NFET} = I_{D,PFET}$$

$$\Rightarrow C_{ox} V_{sat} W_g (1 + \lambda V_{DS}) (V_{gs} - V_{th})$$

same $\left\{ \begin{array}{l} V_{sat,N} = 2 V_{sat,P} \\ W_{g,N} = \frac{1}{2} W_{g,P} \end{array} \right.$

Thus,

$$C_{ox} V_{sat,N} W_{g,N} (1 + \lambda V_{DS,N}) (0.8 - 0.3) = C_{ox} \cdot \frac{1}{2} V_{sat,P} \cdot 2 W_{g,P} (1 + \lambda V_{DS,P}) (0.8 - 0.3)$$

$$\rightarrow \text{All cancelled out} \Rightarrow V_{DS,NFET} = V_{DS,PFET} = 0.8V$$

Because $C_{ox} V_{sat} W_g$ products are same for both Q_1 and Q_2 with same V_{gs} , they have same as 0.8V.

$$\boxed{\therefore V_{out} = V_{DS} = 0.8V} \leftarrow \text{DC Value of } V_{out}$$

To obtain drain current I_D , we need to calculate C_{ox} value.

$$\Rightarrow C_{ox} = \frac{\epsilon_0 \epsilon_r^{3.8}}{t_{ox}} = \frac{3.8 \times 8.85 \times 10^{-12} \text{ F/m}}{0.8 \text{ nm}} = 0.042 \text{ F/m}^2 = 42 \text{ fF}/\mu\text{m}^2$$

⇒ $C_{ox} V_{sat} W_g$ products for PFET & NFET are same!

$$C_{ox} V_{sat} W_g = \left(\frac{42 \text{ fF}}{\mu\text{m}} \right) \left(10^7 \frac{\text{cm}}{\text{s}} \right) \left(\frac{5 \mu\text{m}}{1 \mu\text{m}} \right) = \left(\frac{42 \times 10^{-15}}{10^{-6}} \right) \left(10^7 \cdot 10^2 \frac{\text{m}}{\text{s}} \right) \cdot 5$$

$$= \underline{21 \text{ mA/V}}$$


⇒ Drain Current

$$I_{D,NFET} = I_{D,PFET} = C_{ox} V_{sat} W_g (1 + \lambda V_{DS,N}) (V_{GS} - V_{th})$$

$$= 21 \text{ mA/V} \cdot (1 + 0.3 \text{ V}^{-1} \cdot 0.8 \text{ V}) (0.8 \text{ V} - 0.3 \text{ V})$$

$$\therefore \boxed{I_D = 13.02 \text{ mA}}$$

(c,d)

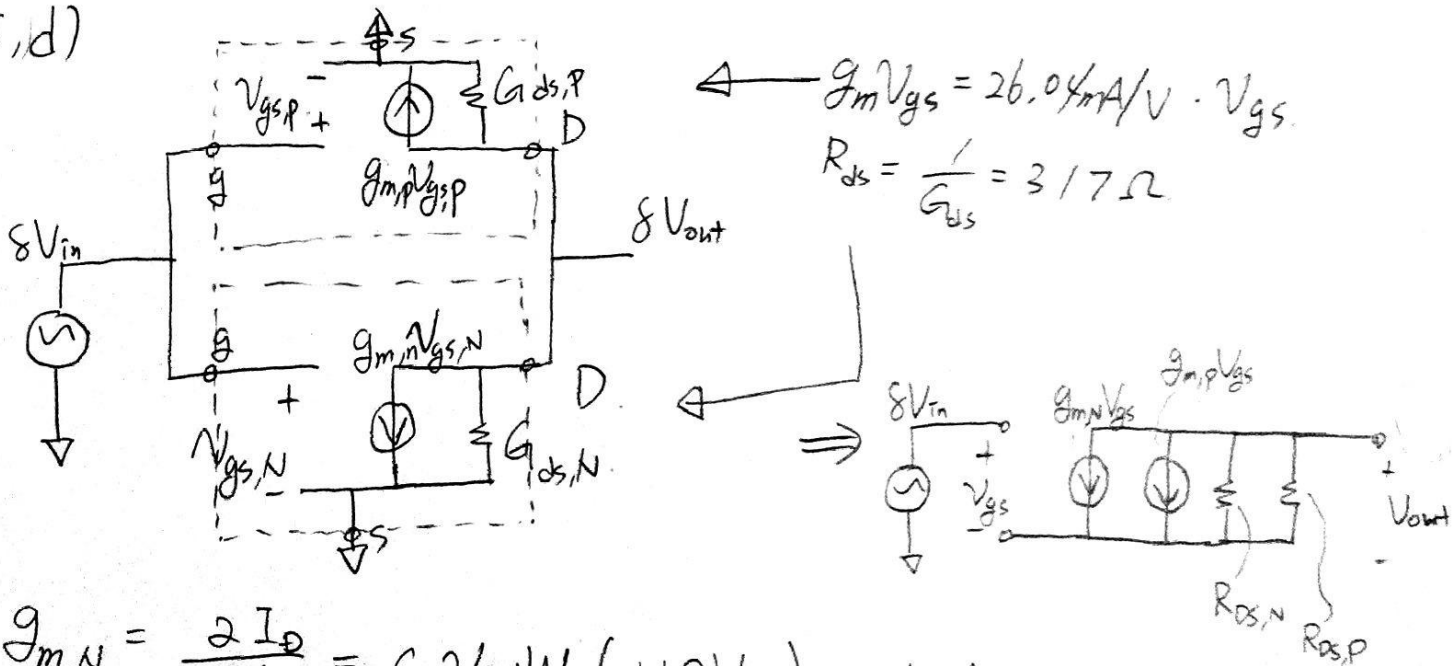

$$g_m V_{gs} = 26.04 \text{ mA/V} \cdot V_{gs}$$

$$R_{ds} = \frac{1}{G_{ds}} = 317 \Omega$$

$$g_{m,N} = \frac{2 I_D}{2 \frac{V_{GS}}{\text{DC } V_{GS}}} = C_{ox} V_{sat} W_g (1 + \lambda V_{DS}) = 21 \frac{\text{mA}}{\text{V}} \cdot (1 + 0.3 \cdot 0.8) = \boxed{26.04 \text{ mA/V}}$$

$$R_{ds,N} = \frac{1}{G_{ds}} = \frac{1}{\left(\frac{2 I_D}{2 V_{DS}} \right)} = \frac{1}{\left(\frac{\lambda I_D}{1 + \lambda V_{DS}} \right)} = \frac{(1 + \lambda V_{DS})}{\lambda (C_{ox} V_{sat} W_g (1 + \lambda V_{DS}) (V_{GS} - V_{th}))}$$

$\frac{1}{0.3 \text{ V}^{-1}} \quad \uparrow \quad \uparrow \quad \uparrow$
 $21 \text{ mA} \quad I_D \quad 0.8 - 0.3$

$$= \boxed{317 \Omega}$$

Q_1 & Q_2 have same characteristics,

$$\left. \begin{aligned} g_{m,N} &= g_{m,P} = 26.04 \text{ mA/V} \\ R_{ds,N} &= R_{ds,P} = 317 \Omega \end{aligned} \right\}$$

(e)


AC voltage : δV_{in}

$$\Rightarrow V_{DC+AC} = 0.8V + \delta V_{in}$$

For small signal analysis,

&

For equivalent circuit,

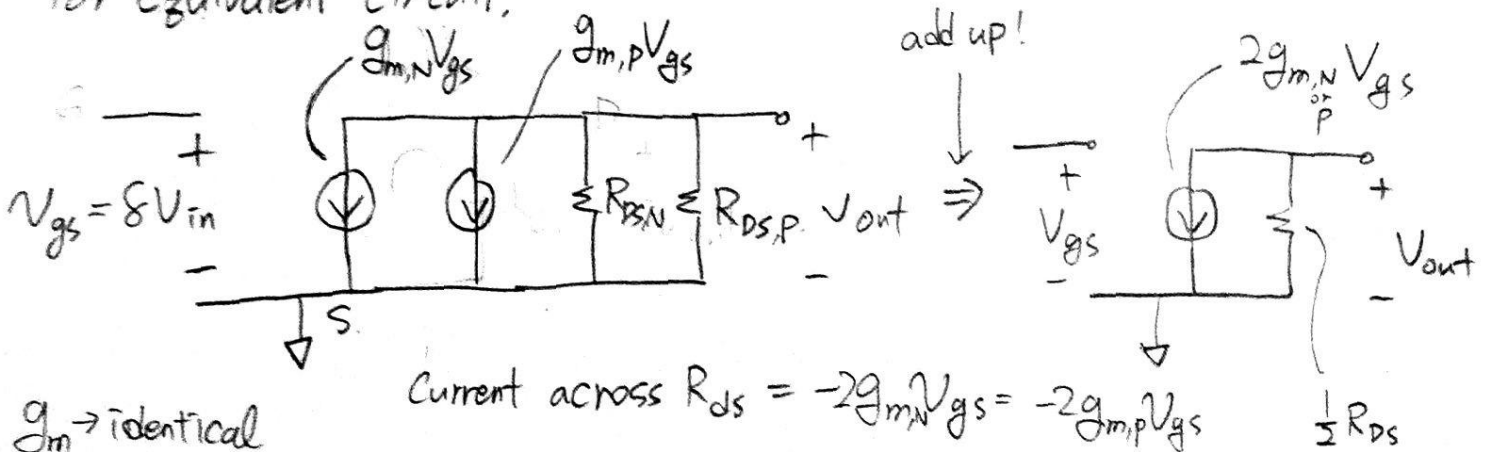

Current across $R_{ds} = -2g_{m,N}V_{gs} = -2g_{m,P}V_{gs}$

$g_m \rightarrow$ identical

$R_{ds} = \frac{1}{G} \Rightarrow$ identical

for both N & P FET

\therefore Thus,

$$V_{out} = -g_m V_{gs} R_{ds}$$

$$= -26.04 \text{ mA/V} \cdot \delta V_{in} \cdot 317 \Omega$$

$$= \underline{\underline{8.25 \delta V_{in}}}$$

#4

$$I_a = k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2}$$

(a)

$$\text{Output Conductance} = \frac{\partial I_a}{\partial V_a} = \frac{\partial}{\partial V_a} \left[k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2} \right]$$

$$G_m = \frac{3}{2} \frac{k_p}{\mu} \left(V_g + \frac{V_a}{\mu} \right)^{1/2}$$

$$\text{Transconductance} = \frac{\partial I_a}{\partial V_g} = \frac{\partial}{\partial V_g} \left(k_p \left(V_g + \frac{V_a}{\mu} \right)^{3/2} \right)$$

$$g_m = \frac{3}{2} k_p \left(V_g + \frac{V_a}{\mu} \right)^{1/2}$$

(b)

To get k_p, μ values, pick some data from graph.

By graph,

① At $V_g = 0V, V_a = 200V, I_a = 4.5mA$

$$\rightarrow I_a = 4.5mA = k_p \left(\frac{200}{\mu} \right)^{3/2} \rightarrow (4.5mA)^2 = k_p^2 \left(\frac{200}{\mu} \right)^3$$

② At $V_g = -2V, V_a = 200V, I_a = 0.5mA$

$$\rightarrow I_a = 0.5mA = k_p \left(-2 + \frac{200}{\mu} \right)^{3/2} \rightarrow (0.5mA)^2 = k_p^2 \left(\frac{200}{\mu} - 2 \right)^3$$

$$\Rightarrow \left(\frac{4.5mA}{0.5mA} \right)^2 = \frac{k_p^2}{k_p^2} \left(\frac{\frac{200}{\mu}}{\frac{200}{\mu} - 2} \right)^3 \Rightarrow 81 = \left(\frac{200}{200 - 2\mu} \right)^3$$

$$(81)^{1/3} = \frac{200}{200 - 2\mu}$$

$$\rightarrow \frac{200}{(81)^{1/3}} = 200 - 2\mu \Rightarrow \mu = 100 - \frac{100}{(81)^{1/3}} = \underline{76.888}$$

Q

$$\therefore k_p = \frac{4.5 \times 10^{-3} \text{ A}}{\left(\frac{200}{76.888}\right)^{3/2}} = \underline{0.001115 \text{ A/V}^{3/2}}$$

Thus,

$$\text{At } V_a = 200 \text{ V, } V_g = -0.5 \text{ V}$$

Transconductance

$$g_m = \frac{3}{2} k_p \left(-0.5 + \frac{200}{\mu}\right)^{1/2} = 0.0035 \text{ A/V} = \underline{3.5 \text{ mA/V}}$$

Output Conductance & slope of the graph

$$G = \frac{3}{2} \frac{k_p}{\mu} \left(-0.5 + \frac{200}{\mu}\right)^{1/2} = 0.000046 \text{ A/V} = \underline{0.046 \text{ mA/V}}$$

#5.

(a) Using the work from #4,

given $V_{inDC} = V_g = -0.5V$ & $V_a = V_{AA} - I_a \cdot R_L = 232 - 10 \cdot 10^{-3} I_a$

For satisfying value, $V_a = 200V$


$I_a = 3.2mA$

As also mentioned, taking same tube in #4b,

$g_m = 3.5/mA/V$

$G = 0.046mA/V \rightarrow R_{DS} = \frac{1}{G} = 21.74k\Omega$

(b) small signal equivalent circuit

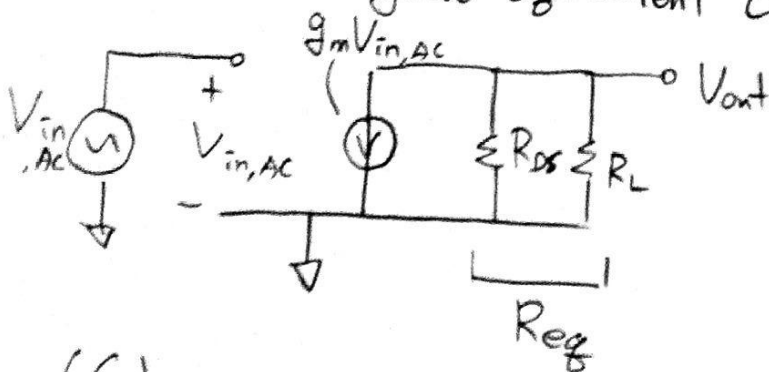

(c)


We can combine R_{DS} & $R_L \Rightarrow R_{eq} = R_{DS} // R_L$ & Let $V_{inAC} = \pm 1mV$,
 $= \left(\frac{217.4}{21.74+10} \right) k\Omega = 6.85k\Omega$

Thus,

$$V_{out} = -g_m V_{inAC} (R_{DS} // R_L) = -3.5/mA/V (\pm 1mV) \cdot 6.85k\Omega \rightarrow \frac{V}{A}$$

$$= \pm 24.04mV$$

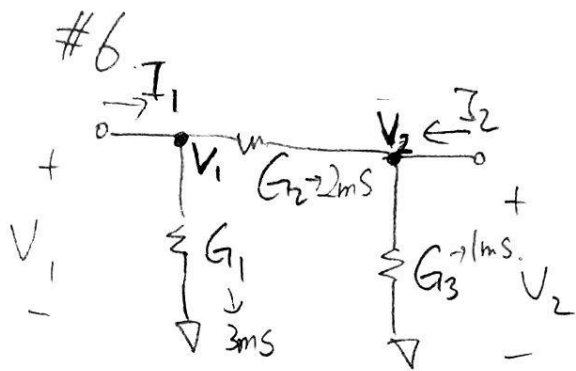$\therefore V_{outAC} = -24.04mV \cdot \cos(2\pi \cdot 1kHz \cdot t)$



$$I_1 = G_1 V_1 + G_2 (V_1 - V_2) = (G_1 + G_2) V_1 - G_2 V_2$$

$$I_2 = G_3 V_2 + G_2 (V_2 - V_1) = -G_2 V_1 + (G_2 + G_3) V_2$$

(a)


$$\Rightarrow Y = \begin{pmatrix} 5 \text{ mS} & -2 \text{ mS} \\ -2 \text{ mS} & 3 \text{ mS} \end{pmatrix} \Rightarrow \mathbf{I} = \mathbf{Y} \mathbf{V}$$

$$\Rightarrow \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

(b)

$$\mathbf{Y}^{-1} \mathbf{I} = \mathbf{V} \Rightarrow \mathbf{Z} = \mathbf{Y}^{-1} = \frac{1}{ad-bc} \begin{pmatrix} d & -b \\ -c & a \end{pmatrix} = \frac{1}{(5-4) \times 10^{-6}} \begin{pmatrix} 3 \times 10^{-3} \Omega & 2 \times 10^{-3} \Omega \\ 2 \times 10^{-3} \Omega & 5 \times 10^{-3} \Omega \end{pmatrix}$$
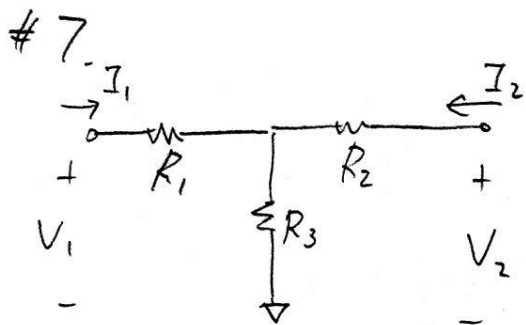
$$\therefore \mathbf{Z} = \frac{1}{1} \begin{pmatrix} 3 \text{ k}\Omega & 2 \text{ k}\Omega \\ 2 \text{ k}\Omega & 5 \text{ k}\Omega \end{pmatrix}$$



$$\Rightarrow V_1 = I_1 R_1 + (I_1 + I_2) R_3 = (R_1 + R_3) I_1 + R_3 I_2$$

$$V_2 = I_2 R_2 + (I_1 + I_2) R_3 = I_1 R_3 + (R_2 + R_3) I_2$$



(b) $\Rightarrow \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$

$$\mathbf{Z} = \begin{pmatrix} 4 \text{ k}\Omega & 1 \text{ k}\Omega \\ 1 \text{ k}\Omega & 3 \text{ k}\Omega \end{pmatrix}$$

(a)

$$\therefore \mathbf{Y} = \mathbf{Z}^{-1} = \frac{1}{11 \times 10^{-6}} \begin{pmatrix} 3 \times 10^3 & -1 \times 10^3 \\ -1 \times 10^3 & 4 \times 10^3 \end{pmatrix} = \frac{1}{11} \begin{pmatrix} 3 \text{ mS} & -1 \text{ mS} \\ -1 \text{ mS} & 4 \text{ mS} \end{pmatrix}$$

#8.

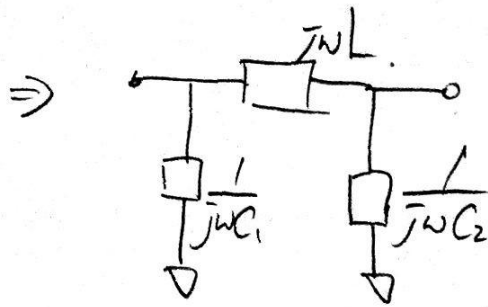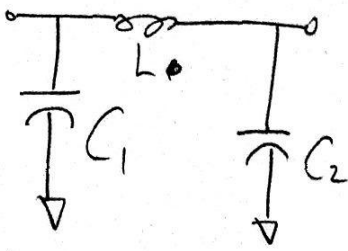

$f = 2 \text{ GHz}$
 $C_1 = 2 \text{ pF}$
 $C_2 = 3 \text{ pF}$
 $L = 2 \text{ nH}$

by following #6.

$$Y = \begin{pmatrix} \frac{1}{j\omega C_1} + j\omega L & -j\omega L \\ -j\omega L & \frac{1}{j\omega C_2} + j\omega L \end{pmatrix} = j \begin{pmatrix} \omega L - \frac{1}{\omega C_1} & -\omega L \\ -\omega L & \omega L - \frac{1}{\omega C_2} \end{pmatrix}$$

For ωL

$$\rightarrow 2\pi f L = 2\pi \times 2 \times 10^9 \times 2 \times 10^{-9} = 8\pi = \underline{25.13}$$

$$Y = j \begin{pmatrix} -14.656 & -25.13 \\ -25.13 & -1.393 \end{pmatrix}$$