

$$I_D = \frac{\mu C_{ox} W_{eff}}{2L_g} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds}), \quad v_D > v_G - v_{th}$$

$$I_D = \frac{\mu C_{ox} W_{eff}}{2L_g} [2(V_{gs} - V_{th})V_{ds} - V_{ds}^2] (1 + \lambda V_{ds}), \quad v_D < v_G - v_{th}$$

* $\frac{\mu C_{ox}}{2L_g} = \frac{1 \text{ mA}}{1 \text{ } \mu\text{m}^2 \text{ V}^2}$, $\lambda = 0 \text{ V}^{-1}$, $W_{g1} = 1 \text{ } \mu\text{m}$, $V_{DD} = 3.3 \text{ V}$, $V_{th} = 0.3 \text{ V}$

a) R_{ref} ST $I_{D1} = 100 \text{ } \mu\text{A}$

$$I_{D1} = \frac{\mu C_{ox}}{2L_g} W_{g1} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$0.1 \text{ mA} = \left(\frac{1 \text{ mA}}{1 \text{ } \mu\text{m}^2 \text{ V}^2} \right) (1 \text{ } \mu\text{m}) (V_{gs} - 0.3 \text{ V})^2 \Rightarrow V_{gs} = 0.616 \text{ V}$$

$$\text{so } R_{ref} = \frac{V_{DD} - V_{ds}}{I_{D1}} = \frac{(3.3 - 0.616) \text{ V}}{0.1 \text{ mA}} = \boxed{26.84 \text{ k}\Omega = R_{ref}}$$

b) assume $R_L \approx 0$, find W_{g2} ST $I_{D2} = 300 \text{ } \mu\text{A}$

$$0.3 \text{ mA} = \left(\frac{1 \text{ mA}}{1 \text{ } \mu\text{m}^2 \text{ V}^2} \right) W_{g2} (0.616 \text{ V} - 0.3 \text{ V})^2 \Rightarrow \boxed{W_{g2} = 3.004 \text{ } \mu\text{m}}$$

c) Constant current operation when Q point stays in saturation region.

so const. current when $V_{ds} \geq V_{ds}^{sat}$ + when $R_L \leq \frac{V_{ds}^{sat}}{I_D} = 50 \text{ } \mu\text{A}$

$$V_{ds}^{sat} = V_{gs} - V_{th} = 0.616 \text{ V} - 0.3 \text{ V} = 0.316 \text{ V}$$

so

$$\boxed{\begin{aligned} V_D &\geq 0.316 \text{ V} \\ + \\ R_L &\leq 6.32 \text{ k}\Omega \end{aligned}}$$

② now set $\lambda = 0.1 \text{ V}^{-1}$

a) Find R_{ref} ST $I_{D_1} = 100 \mu\text{A}$

NB: $V_{DS_1} = V_{GS}$, $W_{g_1} = 1 \mu\text{m}$

$$\text{so } I_{D_1} = \frac{\mu C_{\text{ox}}}{2L_g} W_{g_1} (V_{GS} - V_{th})^2 (1 + \lambda V_{GS})$$

$$0.1 \text{ mA} = \left(\frac{1 \text{ mA}}{1 \text{ mmV}^2} \right) (1 \mu\text{m}) (V_{GS} - 0.3 \text{ V})^2 (1 + (0.1 \text{ V}^{-1}) V_{GS})$$

V_{GS} must be > 0 so only one soln remains:

$$\Rightarrow \boxed{V_{GS} = 0.607 \text{ V}}$$

b) now $I_{D_2} = \frac{\mu C_{\text{ox}}}{2L_g} W_{g_2} (V_{GS} - V_{th})^2 (1 + \lambda (V_{DD} - I_{D_2} R_L))$

where we've substituted $V_{DS_2} = V_{DD} - I_{D_2} R_L$

R_L is assumed to be small, so $V_{DS_2} = V_{DD} = 3.3 \text{ V}$

$$\text{so } 0.3 \text{ mA} = \left(\frac{1 \text{ mA}}{1 \text{ mmV}^2} \right) W_{g_2} (0.607 \text{ V} - 0.3 \text{ V})^2 (1 + (0.1) \cdot (3.3 \text{ V})^{[\text{V}^{-1}]})$$


find

$$\boxed{W_{g_2} = 2.39 \mu\text{m}}$$

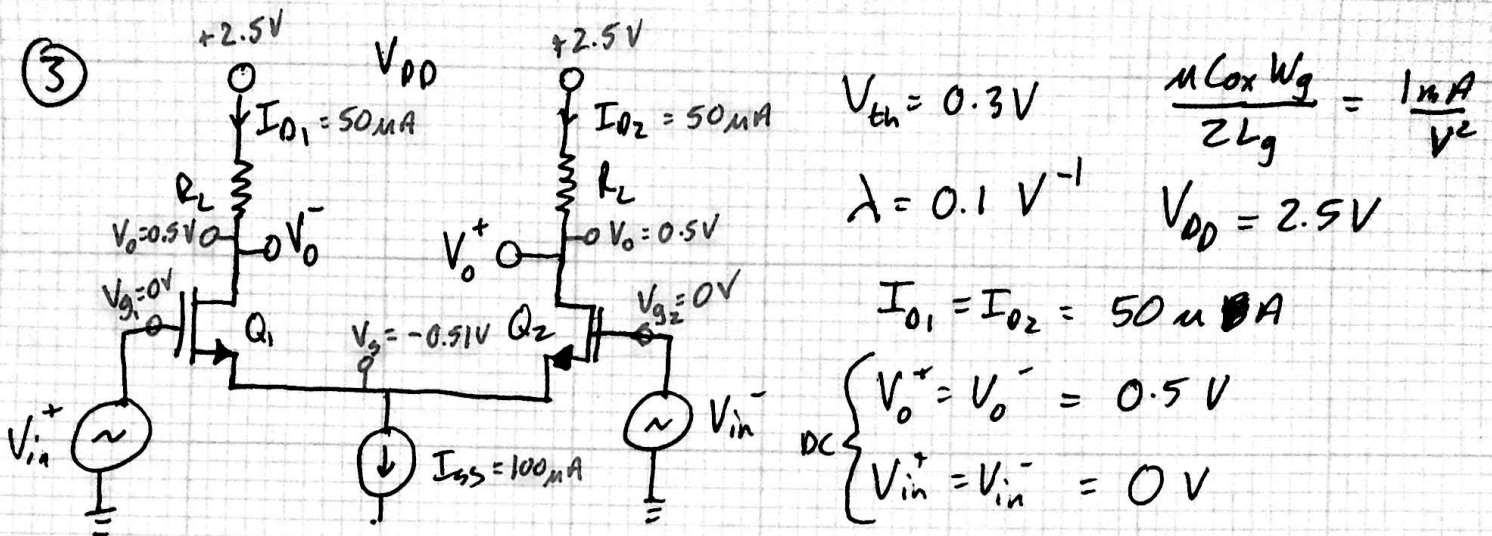c) now let $V_{D_2} = 2.3 \text{ V}$, $V_S = 0 \text{ V}$ so $V_{D_2} = V_{DS_2}$

$$\text{so } I_{D_2} = \left(\frac{1 \text{ mA}}{1 \text{ mmV}^2} \right) (2.39 \mu\text{m}) (0.607 \text{ V} - 0.3 \text{ V})^2 (1 + (0.1 \text{ V}^{-1}) (2.3 \text{ V}))$$

$$\Rightarrow \boxed{I_{D_2} = 277.1 \mu\text{A}}$$



a) $I_{SS} = I_{01} + I_{02} \Rightarrow I_{SS} = 100 \mu A$

$R_L = \frac{V_{DD} - V_{D1}}{I_{01}} = \frac{2.5V - 0.5V}{50 \mu A} \Rightarrow R_L = 40k\Omega$

b) $0.05 mA = \left(\frac{1 mA}{V^2} \right) \left(\underbrace{V_{gs}}_{-V_s} - 0.3V \right)^2 \left(1 + (0.1) \underbrace{V_{Ds}}_{0.5 - V_s} \right)$

$\Rightarrow V_{gs} = V_g - V_s$, $V_g = 0V$ so $V_{gs} = -V_s$

$V_{Ds} = V_D - V_s$, $V_D = 0.5V \Rightarrow V_{Ds} = 0.5 - V_s$

$\Rightarrow V_s = -0.51V$ or $-0.083V$, DC Voltages + currents marked in red, above

c) find $g_m + g_{ds}$ $g_m = 2 \left(\frac{\mu C_{ox} W_g}{2L_g} \right) (V_{gs} - V_{th}) (1 + \lambda V_{Ds})$

$g_m = 2 \left(\frac{1 mA}{V^2} \right) (-0.51V - 0.3V) [1 + (0.1)(1.01V)]$, $g_m \equiv \frac{\partial I_D}{\partial V_{gs}}$



$\Rightarrow g_m = 0.462 mS$

$g_{ds} = \frac{1}{R_{ds}} \approx \lambda I_D = (0.1 V^{-1})(50 \mu A)$

$\Rightarrow g_{ds} = 5 \mu S \Rightarrow R_{ds} = 200k\Omega$

③ (cont)

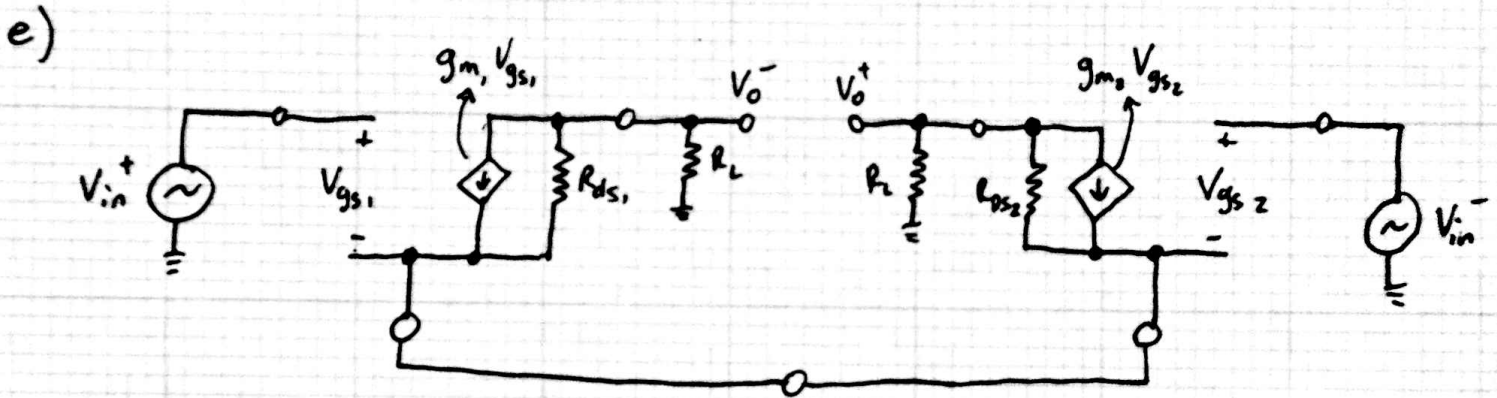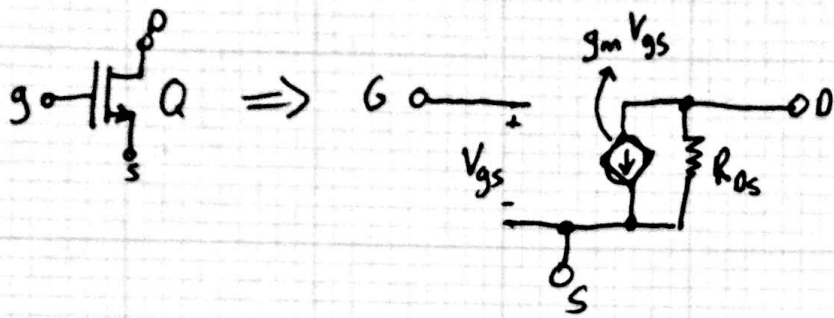d) small sig. equivs of $Q_1 + Q_2$ are identical \therefore due to symmetry so:




f) $V_{in}^+ = (1\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$, $V_{in}^- = (0.5\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$

NB: $V_{in}^+ + V_{in}^-$ are in phase, ~~and the common mode input is~~

$$V_{in}^d = V_{in}^+ - V_{in}^- = (0.5\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$$


$$V_{in}^{cm} = \frac{V_{in}^+ + V_{in}^-}{2} = (0.25\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$$

cm:

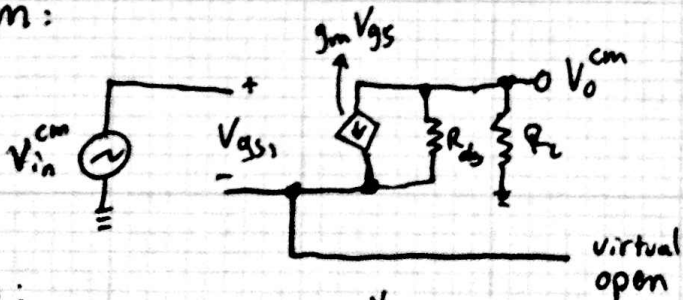

NB: $I_s = 0$ b/c of virtual open
 $\therefore I_D = 0 \Rightarrow A_{cm} = \frac{V_o^{cm}}{V_{in}^{cm}} = 0$

dm:

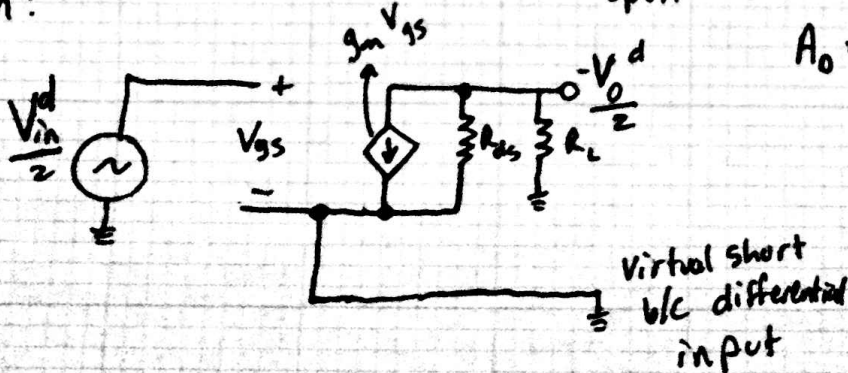

$$A_0 = \frac{V_{out}^d}{V_{in}^d} = g_m (R_L \parallel R_{ds})$$

$$A_0 = (0.462\text{ms}) (40\text{k}\Omega \parallel 200\text{k}\Omega)$$

$$A_0 = 15.4 \quad 33.3\text{k}\Omega$$

③ cont

$$V_{out}^{cm} = A_{cm} V_{in}^{cm} = 0$$

$$V_{out}^d = A_d V_{in}^d = (15.4)(0.5mV) \cos(2\pi \cdot 1kHz \cdot t)$$


$$V_{out}^d = (7.7mV) \cos(2\pi \cdot 1kHz \cdot t)$$

$$V_o^+ = \frac{V_o^d}{2}, \quad V_o^- = -\frac{V_o^d}{2} \Rightarrow$$

$$V_o^+ = (3.85mV) \cos(2\pi \cdot 1kHz \cdot t)$$

$$V_o^- = -(3.85mV) \cos(2\pi \cdot 1kHz \cdot t)$$

④

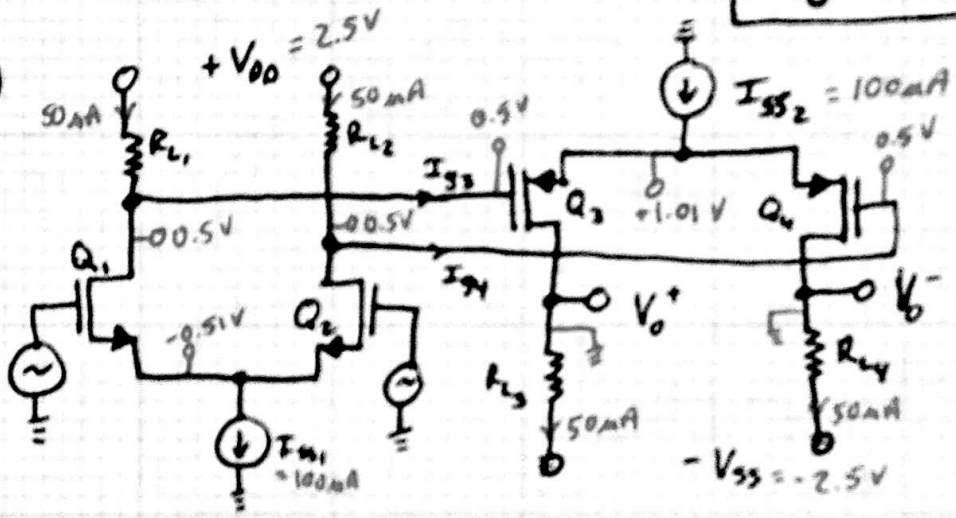

$$\frac{\mu C_{ox} W_g}{2L_g} = 1 \frac{mA}{V^2}$$

$$\lambda = 0.1 V^{-1}$$

NFET: $V_{tn} = 0.3V$
 PFET: $V_{tp} = -0.3V$

$$V_{D1} = V_{D2} = 0.5V$$

$$V_{D3} = V_{D4} = 0.0V$$

$$I_{D1-4} = 50\mu A$$

$$-V_{SS} = -2.5V$$

$$V_{DD} = 2.5V$$

a) we know $I_{S1} = I_{S2} = 0A$

$$I_{S1} = I_{D1} + I_{D2} \Rightarrow I_{S1} = 100\mu A$$

$$I_{S2} = I_{D3} + I_{D4} \Rightarrow I_{S2} = 100\mu A$$

$$R_{L1} = R_{L2} = \frac{V_{DD} - V_{D1,2}}{I_{D1,2}} = \frac{2.5V - 0.5V}{50\mu A} \Rightarrow R_{L1} = R_{L2} = 40k\Omega$$

$$R_{L3} = R_{L4} = \frac{V_{D3,4} - V_{SS}}{I_{D3,4}} = \frac{0V - (-2.5V)}{50\mu A} \Rightarrow R_{L3} = R_{L4} = 50k\Omega$$

b) 1st stage \rightarrow identical to #3 DC bias condns

$$I_{D1,2} = \left(\frac{1mA}{V^2}\right) (V_{S1} - V_{G1} - 0.3V)^2 \left[1 + (0.1V^{-1})(V_{S1} - V_{D1})\right] = 0.05mA$$

$$\Rightarrow V_{S1} = 1.013V$$

⑤



④ cont

c) find g_m, g_{so} for $Q_1 + Q_2$: $g_m = 0.462 \text{ mS}$ from # 3
 $g_{so} = 5 \text{ mS}$

$$g_m = 2 \left(1 \frac{\text{mA}}{\text{V}^2} \right) \left(V_s'' - V_g'' - 0.3 \right) (1 + \lambda(1.01 \text{V})) = 0.462 \text{ mS}$$

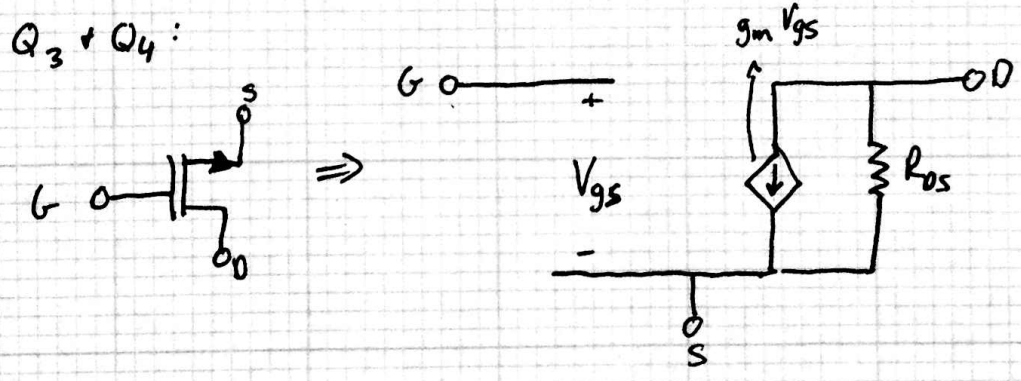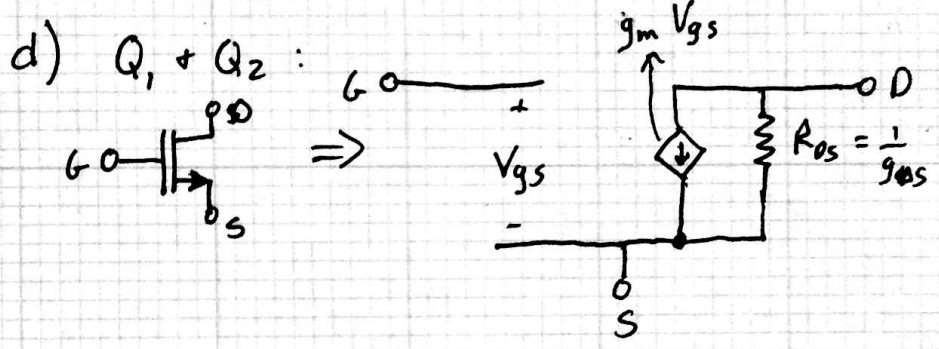1.013 0.5


for $Q_3 + Q_4$: $g_m = 0.462 \text{ mS}$
 $g_{os} = 5 \text{ mS}$



same as nmos b/c $V_{gs} < 0$ changes direction of controlled current source ST I_D flows from Source \rightarrow drain

4) cont

e)

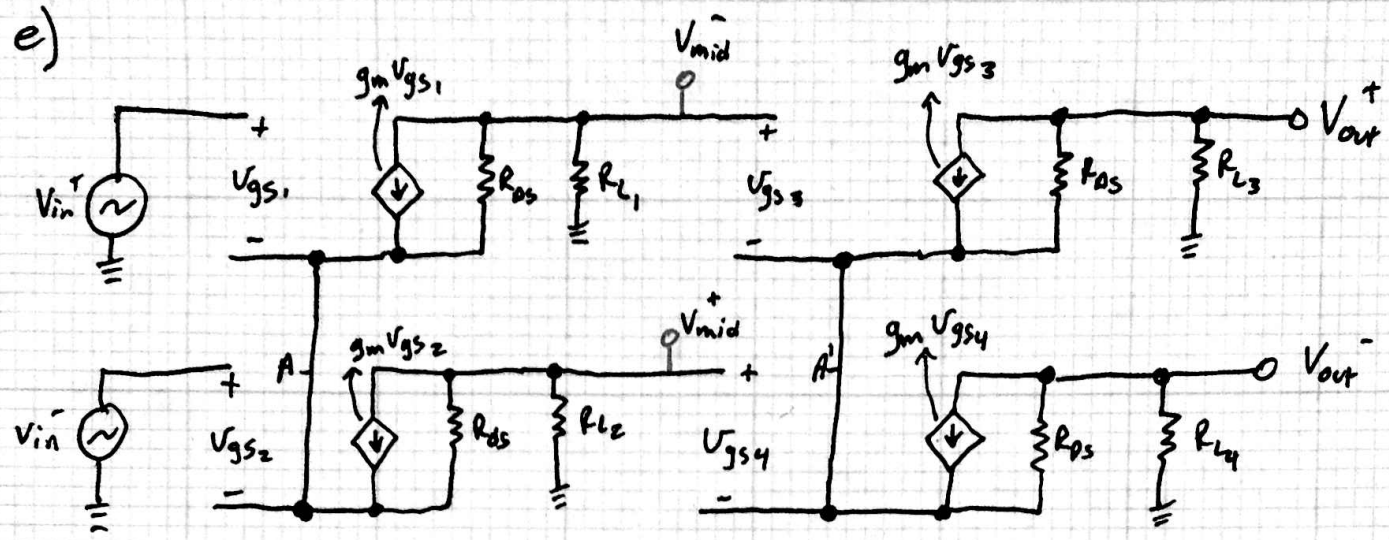

F) $V_{in}^+ = (1\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$

$V_{in}^- = (0.5\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$


NB: $V_{mid}^{+,-}$ are equivalent to $V_o^{+,-}$ in problem #3

for Common Mode input, A & A' are virtual open circuits

so clearly, as in #3, $\frac{V_o^{cm}}{V_{in}^{cm}} = 0$

for differential input:

∵ differential input is anti-symmetric with the ckt symmetry, the voltages at A & A' must be zero, i.e. a virtual ground so we consider only the left half ckt:

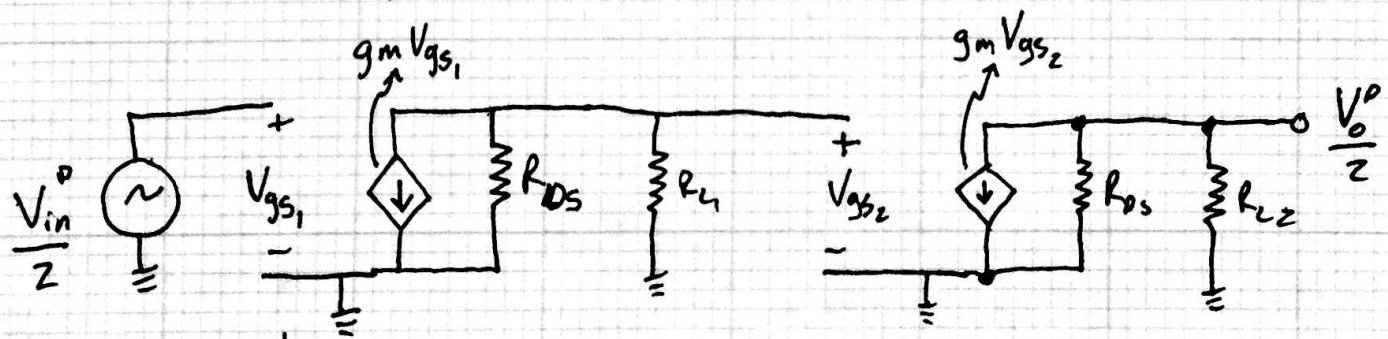

Stage 1: $\frac{V_o^d}{V_{in}^d} = g_m(R_{ds} \parallel R_{L1}) = A_{V1} = 15.4$

$\Rightarrow A_{tot} = A_{V1} A_{V2}$

Stage 2: $\frac{V_o^d}{V_{in}^d} = g_m(R_{ds} \parallel R_{L2}) = A_{V2} = 18.48$

$A_{tot} = 284.6$

④ cont


$$V_o^d = A_{tot} V_{in}^d = (284.6)(0.5 \cos(2\pi \cdot 1\text{kHz} \cdot t))$$

$$V_o^d = (142\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$$

$$V_o^+ = \frac{V_o^d}{2}, \quad V_o^- = -\frac{V_o^d}{2} \Rightarrow$$

$$V_o^+ = (71\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$$
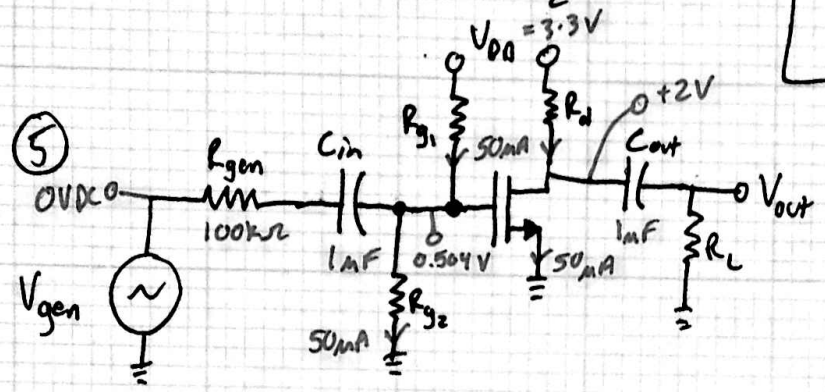
$$V_o^- = -(71\text{mV}) \cos(2\pi \cdot 1\text{kHz} \cdot t)$$



$$\frac{\mu C_{ox} W_g}{2L_g} = \frac{1\text{mA}}{V^2}, \quad \lambda = 0.1\text{V}^{-1}, \quad V_{th} = 0.3\text{V}$$

$$I_D = 50\mu\text{A}, \quad I_{R_{g1}} = 50\mu\text{A}$$

$$V_{DD} = 3.3\text{V}, \quad V_o = 2.0\text{V}$$

$$R_L = 4R_d, \quad R_{gen} = 100\text{k}\Omega$$

$$C_{in} = C_{out} = 1\mu\text{F}$$

a)
$$I_0 = \frac{\mu C_{ox} W_g}{2L_g} (V_{gs} - V_{th})^2 (1 + \lambda V_{DS})$$

$$0.050\text{mA} = \left(\frac{1\text{mA}}{V^2}\right) (V_g - 0.3\text{V})^2 [1 + (0.1)(2.0\text{V})]$$

$$V_g = 0.504\text{V} \quad \text{so } \text{[scribble]}$$

$$V_g = V_{DD} \frac{R_{g2}}{R_{g1} + R_{g2}} + (R_{g1} + R_{g2}) = \frac{V_{DD}}{I_{R_{g1}}} = \frac{3.3\text{V}}{0.05\text{mA}} = 66\text{k}\Omega$$

$$0.504\text{V} = \frac{3.3\text{V} R_{g2}}{66\text{k}\Omega} \Rightarrow R_{g2} = 10.08\text{k}\Omega \quad \text{so } R_{g1} = 55.92\text{k}\Omega$$

$$R_d = \frac{V_{DD} - V_o}{I_D} = \frac{3.3\text{V} - 2\text{V}}{0.05\text{mA}} \Rightarrow R_d = 26\text{k}\Omega \quad \text{so } R_L = 104\text{k}\Omega$$

b) see red labels, above



5) cont

c)
$$g_m = 2 \left(\frac{\mu C_{ox} W_g}{2 L_g} \right) (V_{gs} - V_{th}) (1 + \lambda V_{ds})$$


$$g_m = 2 \left(1 \frac{mA}{\sqrt{2}} \right) (0.504V - 0.3V) [1 + (0.1V^{-1})(2.0V)]$$

$$\Rightarrow \boxed{g_m = 0.4896 \text{ mS}}$$
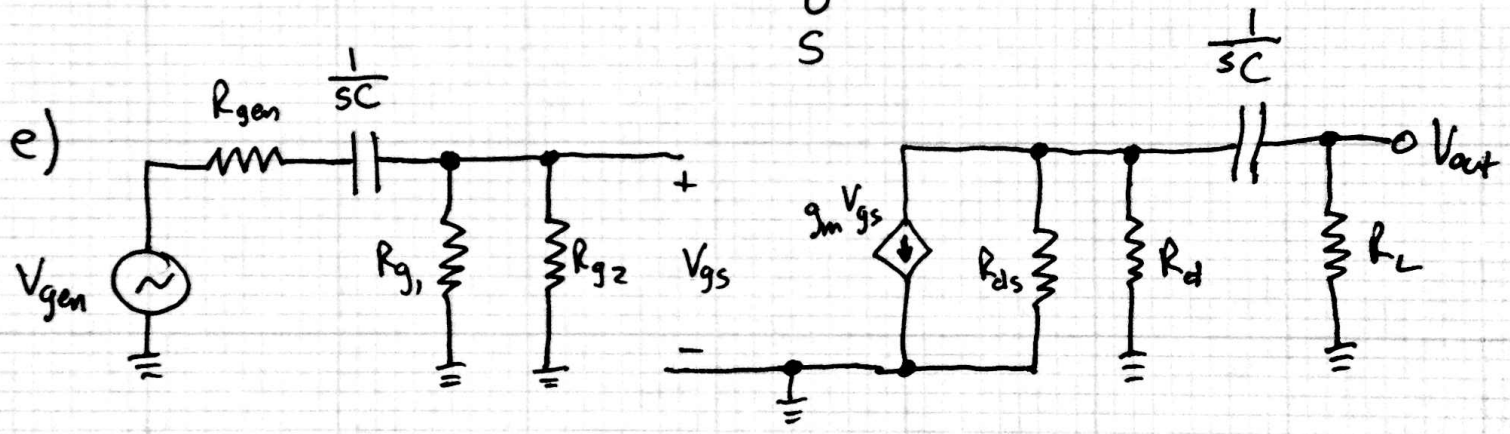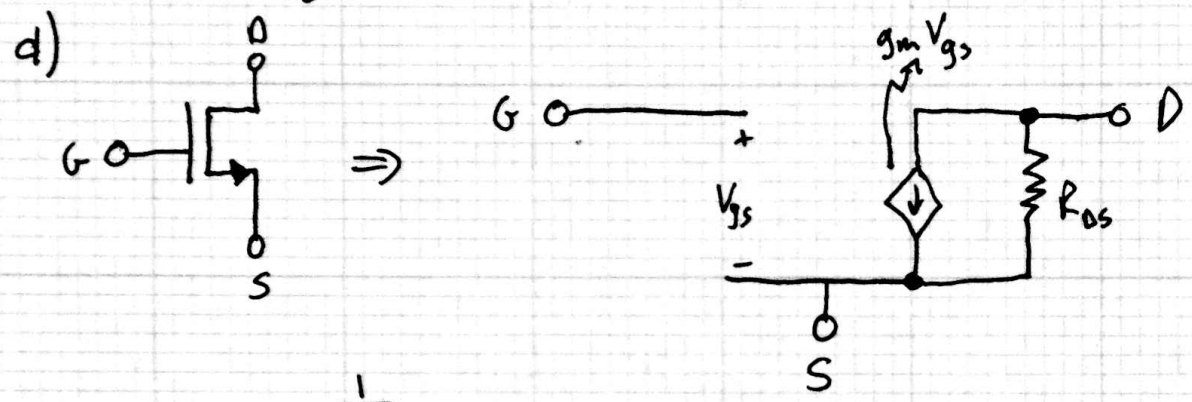
$$g_{ds} = \frac{1}{R_{ds}} \cong \lambda I_0 \Rightarrow \boxed{g_{ds} \cong 5 \mu S}$$



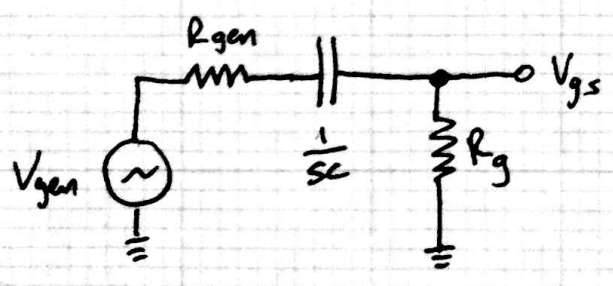f) NB to find $H(s)$ we can split the ckt in half:




$$R_g = R_{g1} \parallel R_{g2}$$

$$\frac{V_{gs}}{V_{gen}} = \frac{R_g}{R_g + R_{gen}} \cdot \frac{sC (R_g + R_{gen})}{1 + sC (R_{gen} + R_g)}$$

⑤ cont

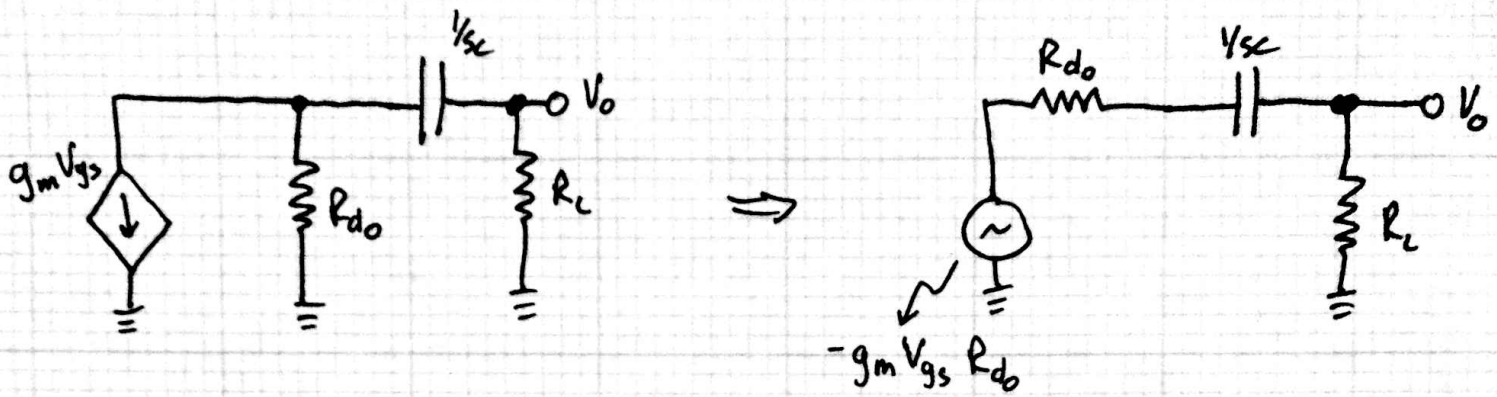and for the right half, use Norton \rightarrow Thevenin transform:



where $R_{do} = R_{ds} \parallel R_d$

$$\text{so } \frac{V_o}{V_{gs}} = -g_m R_{do} \left(\frac{R_L}{R_L + R_{do}} \right) \left(\frac{sC(R_L + R_{do})}{1 + sC(R_L + R_{do})} \right)$$

$$\text{then } H(s) = \frac{V_o}{V_{gen}} = \frac{V_o}{V_{gs}} \cdot \frac{V_{gs}}{V_{gen}}$$

$$H(s) = -g_m R_{do} \left(\frac{R_g}{R_g + R_{gen}} \right) \left(\frac{R_L}{R_L + R_{do}} \right) \left(\frac{s\tau_1}{1 + s\tau_1} \right) \left(\frac{s\tau_2}{1 + s\tau_2} \right)$$

where $\tau_1 \equiv C(R_g + R_{gen})$ + $\tau_2 \equiv C(R_g + R_{gen})$

$R_g \equiv R_{g1} \parallel R_{g2}$, $R_{do} = R_{ds} \parallel R_d$

$$g) \quad \omega_1 \equiv \frac{1}{\tau_1} + \omega_2 \equiv \frac{1}{\tau_2}$$

$$\text{so } f_1 = \frac{1}{2\pi C(R_{g1} \parallel R_{g2} + R_{gen})} = \frac{1}{2\pi (1\mu F)(10k\Omega \parallel 55.9k\Omega + 100k\Omega)}$$

$$f_1 = 1.466 \text{ Hz}$$

$$f_2 = \frac{1}{2\pi C(R_d \parallel R_{os} + R_L)} = \frac{1}{2\pi (1\mu F)(26k\Omega \parallel 20k\Omega + 104k\Omega)}$$

$$f_2 = 1.380 \text{ Hz}$$

⑩

