

# ECE 2C Mid-term Exam B Solutions

Spring 2013

**Problem 1, 15 points**

**Part a, 5 points.**

Q1 is a mobility-limited FET, ie.

$$I_d = (\mu C_{ox} W_g / 2L_s)(V_{gs} - V_{th})^2 (1 + \lambda V_{ds}) \text{ where}$$

$$(\mu C_{ox} W_g / 2L_s) = 1 \text{ mA/V}^2, \lambda = 0.0 \text{ V}^{-1}, \text{ and } V_{th} = 0.3 \text{ V.}$$

$$V_{DD} = 5 \text{ Volts}$$

The drain is biased at +3.0 Volts.

The drain current is 0.25 mA.

The DC current in  $R_{G1}$  is 50  $\mu\text{A}$

Find  $R_{G1}$ ,  $R_{G2}$ ,  $R_D$ , and the DC gate voltage.

$$R_{G1} = \frac{16 \text{ k}\Omega}{0.8} \quad R_{G2} = \frac{84 \text{ k}\Omega}{0.8} \quad R_D = 8 \text{ k}\Omega$$

$$R_D = \frac{5 - 3}{0.25 \text{ mA}} = 8 \text{ k}\Omega$$

$$0.25 \times 10^{-3} = 1 \times 10^{-3} (V_{gs} - 0.3)^2$$


$$0.25 = (V_{gs} - 0.3)^2$$

$$0.5 = V_{gs} - 0.3$$

$$V_{gs} = 0.8 \text{ V}$$

$$R_{G1} = \frac{0.8}{(50 \times 10^{-6})} = 16 \text{ k}\Omega$$
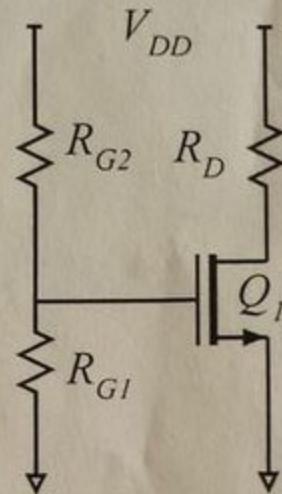
$$R_{G2} = \frac{5 - 0.8}{(50 \times 10^{-6})} = 84 \text{ k}\Omega$$




Part b, 5 points

Using the FET parameters and DC bias conditions of part (a), draw a small-signal model of the FET and give numerical values of all small-signal parameters.

$$V_g = 0.8 \text{ V}$$

$$\begin{aligned} g_m &= \frac{\partial I_D}{\partial V_{GS}} = \frac{1 \text{ mA}}{\sqrt{2}} (2)(V_{GS} - V_{th}) \\ &= \frac{2 \text{ mA}}{\sqrt{2}} (0.5) \\ &= 1 \text{ mS} \end{aligned}$$
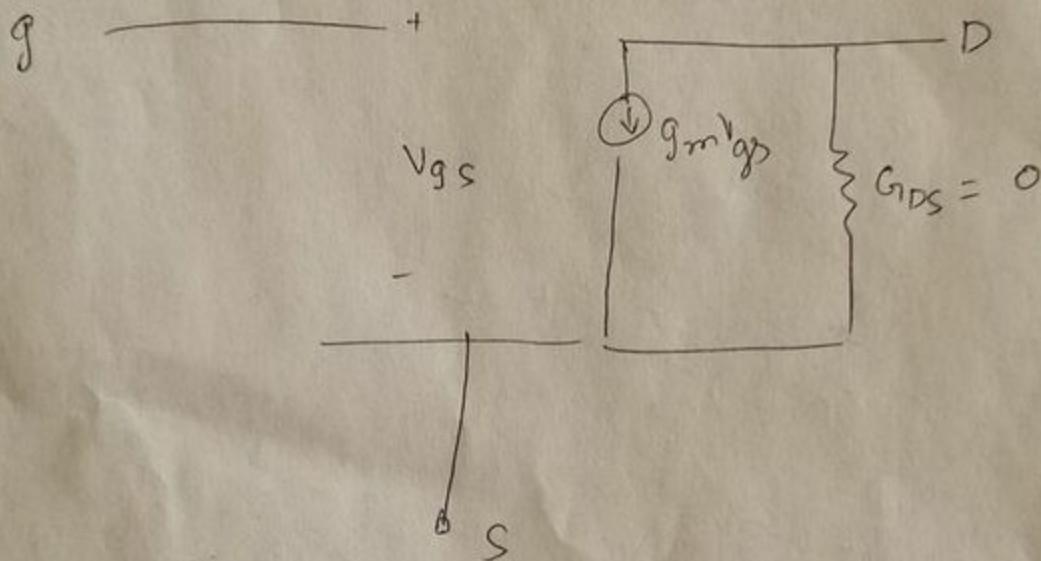
$$G_{DS} = \frac{\partial I_D}{\partial V_{DS}} = 0 \quad \text{since } \lambda = 0$$




1) (c)

$$I_C = k (V_{be} - \phi)^2$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{k}{\beta} (V_{be} - \phi)^2$$
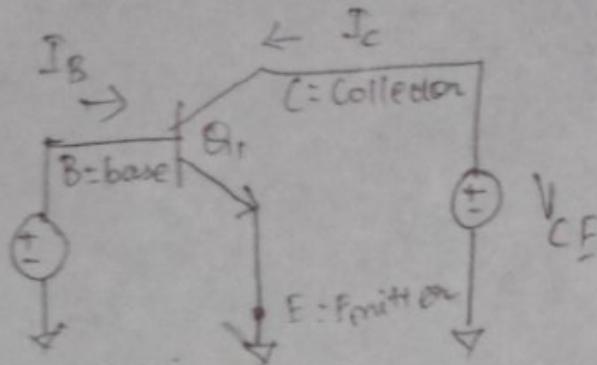
$$k = 2 \text{ mA/V}^2, \quad \phi = 0.9 \text{ V}, \quad \beta = 100$$



Small signal parameters are

$$G_{111} = \frac{\partial I_B}{\partial V_{be}} = \frac{2k}{\beta} (V_{be} - \phi)$$

$$= \frac{2 \times 2 \text{ mA}}{\text{V}^2} (1.1 - 0.9)$$

$$= \frac{100}{(8 \times 10^3) \text{ mA}}$$

$$= 8 \mu\text{s}$$

$$= \frac{1}{(125 \times 10^3) \text{ s}}$$

$$G_{112} = \frac{\partial I_B}{\partial V_{ce}} = 0$$


$$G_{121} = \frac{\partial I_C}{\partial V_{be}} = \frac{2k(V_{be} - \phi)}{\text{V}}$$

$$= 2 \times 2 \times (1.1 - 0.9) \frac{\text{mA}}{\text{V}}$$

$$= 0.8 \text{ mS}$$

$$G_{T22} = \frac{\partial I_C}{\partial V_{CE}} \approx 0$$

Small signal model is

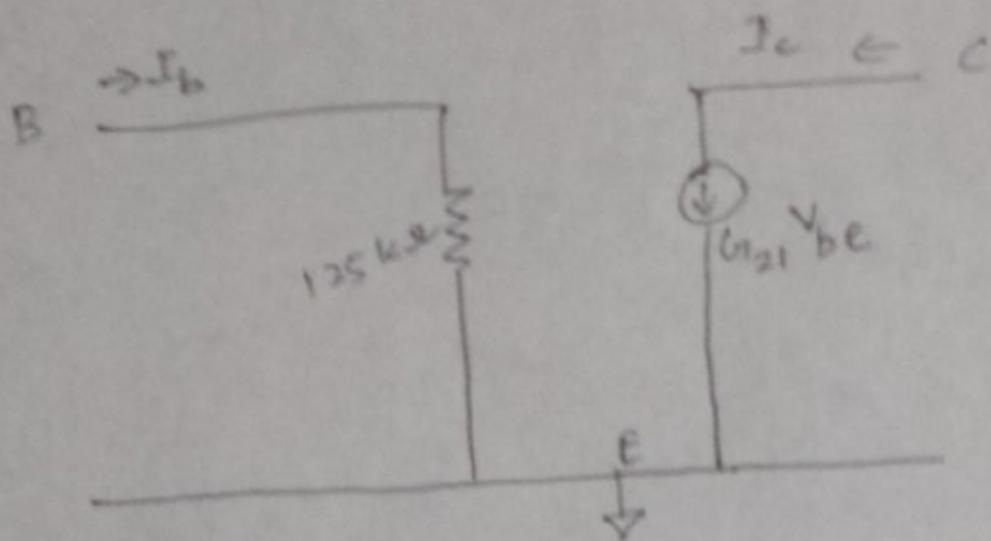

**Problem 2, 15 points**

Q1 is a mobility-limited FET, ie.


$$I_d = (\mu C_{ox} W_g / 2L_g)(V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

where  $(\mu C_{ox} W_g / 2L_g) = 1 \text{ mA/V}^2$ ,

$\lambda = 0.1 \text{ V}^{-1}$ , and  $V_{th} = 0.3 \text{ V}$ .

$$V_{DD} = 5 \text{ Volts}$$

$$R_D = 10 \text{ k}\Omega$$

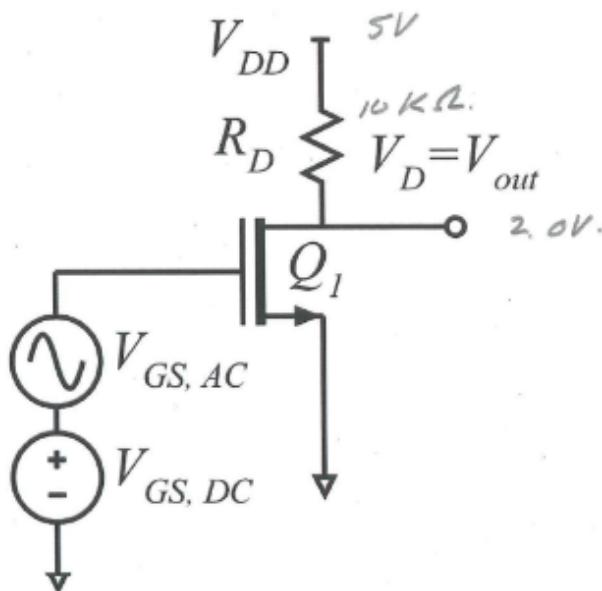

Part a, 5 points

We wish to have a DC drain voltage of 2.0 Volts.

What DC gate-source voltage does this require?

$$V_{GS,DC} = \underline{\underline{0.8V}}$$

$$2 \quad \left[ I_D = \frac{5V - 2V}{10k\Omega} = \frac{3V}{10k\Omega} = 0.3 \text{ mA} \right]$$

$$3 \quad \left[ \begin{aligned} I_{dI} &= 0.3 \text{ mA} = \frac{1 \text{ mA}}{\text{V}^2} (V_{gs} - 0.3V)^2 \left( 1 + \frac{V_{ds}}{10V} \right) \\ 0.25 \text{ V}^2 &= (V_{gs} - 0.3V)^2 \rightarrow V_{gs} = 0.8V \end{aligned} \right]$$

Part b, 5 points

$$V_{GS,AC}(t) = 1 \text{ mV} \cdot \cos(2\pi \cdot 1 \text{ kHz} \cdot t)$$

What is the AC drain voltage?

$$\rightarrow V_{D,AC}(t) = \underline{\underline{\quad}}$$


we need ss model (1!)

on to drop

$$\frac{1}{4} \left[ g_m \approx 2(\mu C_{ox} W/L)(V_{GS} - V_{th})(1 + \frac{1}{2}V_{DS}) \right]$$

$$\frac{1}{4} \left[ = \frac{2 \text{ mA}}{\text{V}^2} (0.8 \text{ V} - 0.3 \text{ V}) = \underline{\underline{1 \text{ mA}}} \right]$$
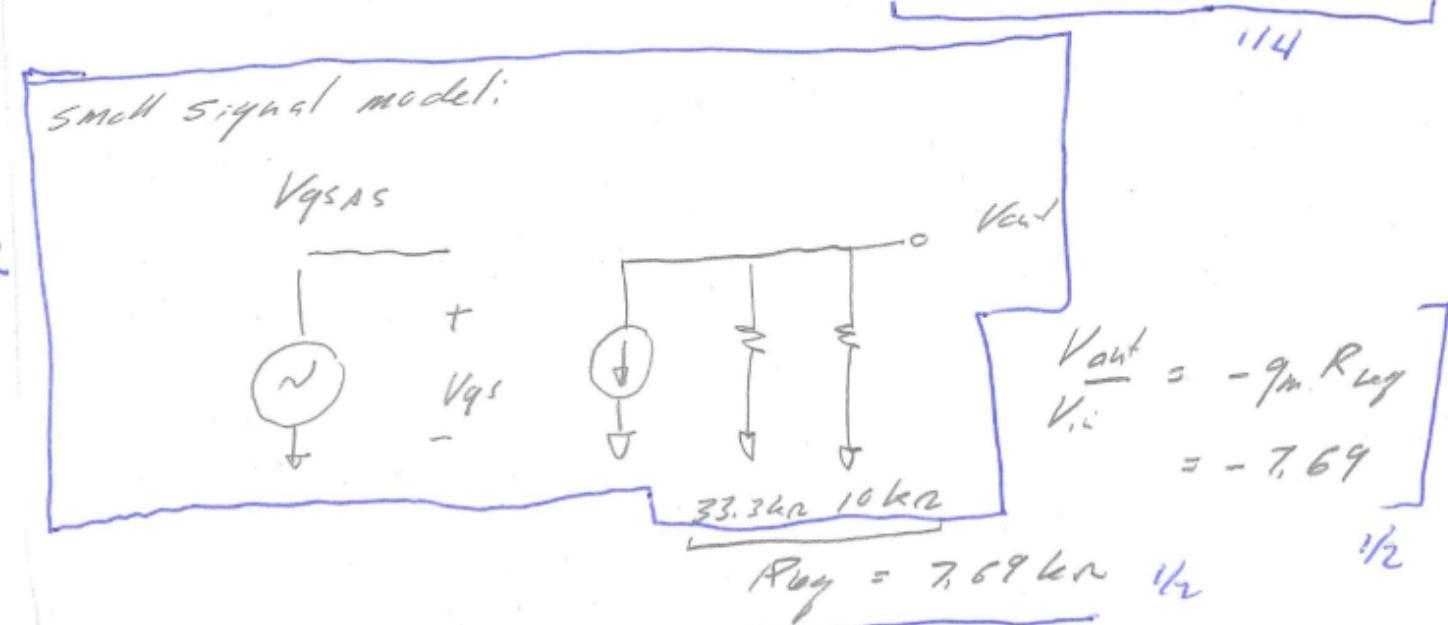
$$\frac{1}{4} \left[ G_{DS} \triangleq \frac{\partial I_D}{\partial V_{DS}} = \frac{1 I_D}{1 + 1 V_{GS}} \approx 1 I_D = \frac{0.3 \text{ mA}}{10 \text{ V}} = 30 \mu \text{A} = \frac{1}{33.3 \text{ k}\Omega} \right]$$




$$1 \left[ V_{out}(t) = -7.69 \text{ mV} \cdot \cos(2\pi \cdot 1 \text{ kHz} \cdot t) \right]$$

### Problem 3, 25 points

You will be working with the circuit at right. Ignore DC bias. You don't need it.


The transistors Q1 and Q2 have transconductances  $g_{m1}$  and  $g_{m2}$ , **both nonzero**, but  $G_{ds1} = G_{ds2} = 0 \text{ mS}$ .

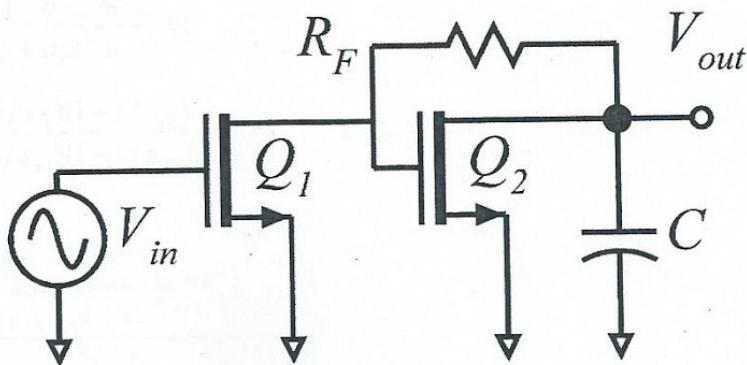The transistors have no gate-source or gate-drain capacitances.


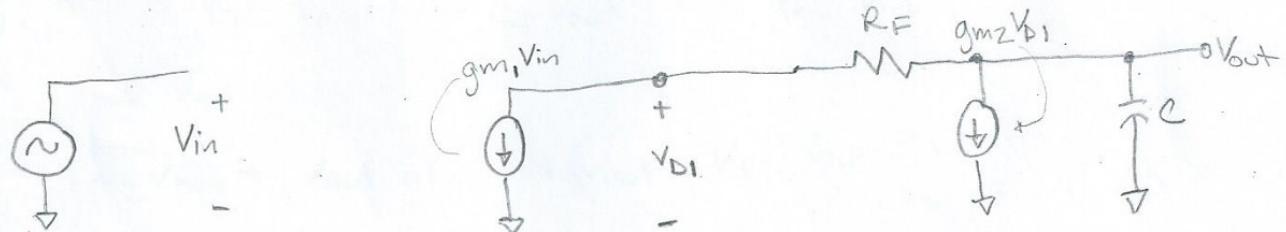
#### Part a, 5 points

replacing the transistors with their small-signal models, draw a small-signal equivalent circuit, labelling all elements and all control voltages.



Part b, 10 points

Compute  $V_{out}(s)/V_{in}(s)$ : The answer must be in one of these two standard forms:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{V_{out}}{V_{in}} \Big|_{\substack{\text{low-frequency} \\ \text{value}}} \times \frac{1 + b_1 s + b_2 s^2 + \dots}{1 + a_1 s + a_2 s^2 + \dots} \quad \text{or}$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{V_{out}}{V_{in}} \Big|_{\substack{\text{low-frequency} \\ \text{value}}} \times \frac{(1 - s/s_{z1})(1 - s/s_{z2}) \dots}{(1 - s/s_{p1})(1 - s/s_{p2}) \dots}$$

$$V_{out}(s)/V_{in}(s) = \frac{g_{m1} (g_{m2} - G_F)}{G_F (g_{m2} + SC)}$$

$$\sum I = 0 @ V_{D1}$$

$$g_{m1} V_{in} + (V_{D1} - V_{out+}) G_F = 0$$

$$\Rightarrow G_F V_{D1} - G_F V_{out+} = -g_{m1} V_{in}$$

$$\sum I = 0 @ V_{out}$$

$$g_{m2} V_{D1} + V_{out} SC + (V_{out} - V_{D1}) G_F = 0$$

$$\Rightarrow (g_{m2} - G_F) V_{D1} + (SC + G_F) V_{out+} = 0$$

$$\begin{bmatrix} G_F & -G_F \\ g_{m2} - G_F & SC + G_F \end{bmatrix} \begin{bmatrix} V_{D1} \\ V_{out+} \end{bmatrix} = \begin{bmatrix} -g_{m1} V_{in} \\ 0 \end{bmatrix}$$

Use Cramer's Rule:

$$\Delta = \begin{vmatrix} G_F & -G_F \\ g_{m2} - G_F & SC + G_F \end{vmatrix} = G_F(SC + G_F) + G_F(g_{m2} - G_F)$$

$$= G_F(SC + g_{m2})$$

(solving for  $V_{out+}$ , so replace 2nd column)

$$N = \begin{bmatrix} G_F & -g_{m1} V_{in} \\ g_{m2} - G_F & 0 \end{bmatrix} = g_{m1} (g_{m2} - G_F) V_{in}$$

$$V_{out} = \frac{N(s)}{D(s)} = \frac{g_{m1}(g_{m2} - G_F)V_m}{G_F(g_{m2} + sC)}$$

$$\frac{V_{out}}{V_m} = H(s) = \frac{g_{m1}(g_{m2} - G_F)}{G_F(g_{m2} + sC)}$$

$$\boxed{\frac{V_{out}(s)}{V_m(s)} = \frac{g_{m1}(g_{m2} - G_F)}{G_F g_{m2} (1 + s \frac{C}{g_{m2}})}}$$

*Friction & The RLC circuit*

Part c, 10 points

Now  $g_{m1} = g_{m2} = 1 \text{ ms}$ ,  $R_f = 10 \text{ k}\Omega$ ,  $C = 1 \text{ nF}$ .

Give the frequencies, in Hz, of any and all poles and zeros. Clearly indicate if any lie in the right half of the S-plane

1st pole frequency = 159 kHz, 2nd pole frequency = \_\_\_\_\_,  
3rd pole frequency = \_\_\_\_\_

1st zero frequency = \_\_\_\_\_, 2nd zero frequency = \_\_\_\_\_,  
3rd zero frequency = \_\_\_\_\_

pole

$$\gamma = \frac{C}{gm_2} = \frac{1 \text{ nF}}{1 \text{ ms}} = 1 \mu\text{s}$$

$$f_{\text{pole}} = \frac{1}{2\pi \cdot \gamma} = \frac{0.159}{1 \mu\text{s}} = 159 \text{ kHz}$$

### Problem 4, 20 points

We have a circuit for which

$$\frac{V_{out}(s)}{V_{in}(s)} = H(s) = H_{DC} \times \frac{\frac{1}{s\tau_1}}{(1+s\tau_2)(1+s\tau_3)} = \frac{1+s/10^7}{(1+s/10^8)(1+s/10^9)}$$

$$\omega_{zero} = 10^7 = 2\pi f_2$$

$$\Rightarrow \omega_{pole1} = 10^8 = 2\pi f_{p1}$$

$$\omega_{pole2} = 10^9 = 2\pi f_{p2}$$

where  $\tau_1 = 100 \text{ ns}$ ,  $\tau_2 = 10 \text{ ns}$ ,  $\tau_3 = 1 \text{ ns}$ .

$$\Rightarrow f_2 = 1.6 \text{ MHz}$$

$$f_{p1} = 16 \text{ MHz}$$


$$f_{p2} = 160 \text{ MHz}$$

} 0.5 pt each = 1.5 pts

#### Part a, 10 points

Make an \*\*accurate\*\* asymptotic Bode plot of  $\|H\|$ , labelling and dimensioning axes and clearly labelling all slopes and all critical frequencies.
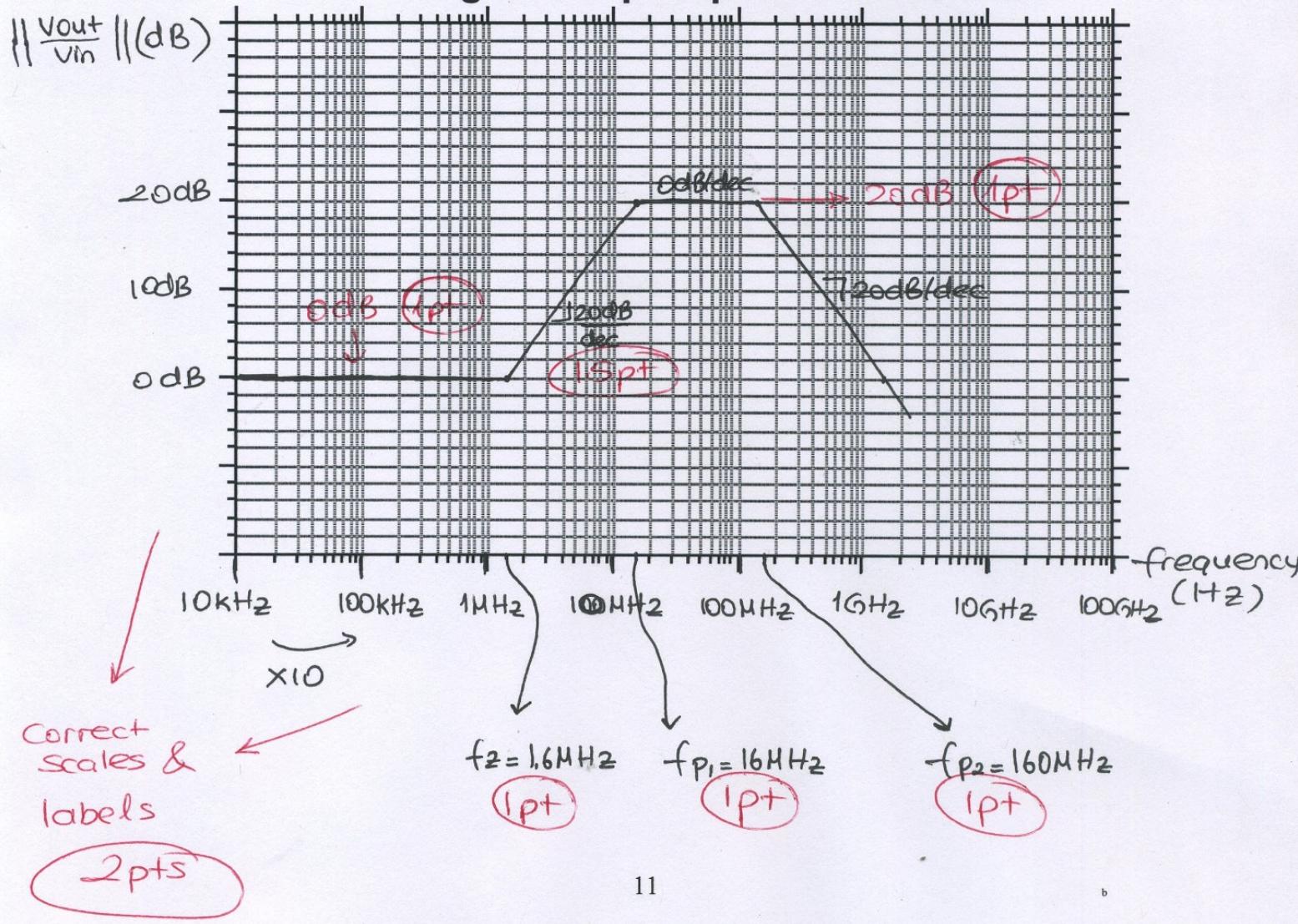
### Bode Magnitude plot-please label axes



**Part b, 10 points**

Make an \*\*accurate\*\* root locus plot of  $H(s)$ , labelling and dimensioning axes and clearly labelling all critical frequencies.

**be sure to label axes with #s and units**

