

1.) LC filter passes 1 GHz component only → find compo with that


a) Find AC voltage @ load

• definition of Fourier series

$$f(t) = a_0 + a_1 \sqrt{2} \cos\left(1 \cdot \frac{2\pi}{T} \cdot t\right) + a_2 \sqrt{2} \cos\left(2 \cdot \frac{2\pi}{T} \cdot t\right) + \dots + b_1 \sqrt{2} \sin\left(1 \cdot \frac{2\pi}{T} \cdot t\right) + b_2 \sqrt{2} \sin\left(2 \cdot \frac{2\pi}{T} \cdot t\right) + \dots$$

• we want to find coefficients $a_0, a_1, \dots, b_1, \dots$
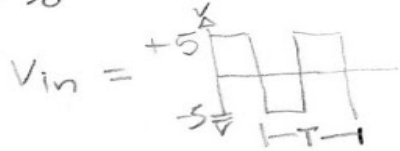
$$a_0 = \frac{1}{T} \int_0^T v_{in}(t) dt$$



$$T = \frac{1}{f} = \frac{1}{1 \text{ GHz}} = 1 \times 10^{-9} \text{ s} = 1 \text{ ns}$$

$$a_0 = \frac{1}{1 \times 10^{-9}} \left[\int_0^{.5 \text{ ns}} 5 dt + \int_{.5 \text{ ns}}^{1 \text{ ns}} -5 dt \right] = 0$$

$$a_1 = \frac{1}{T} \int_0^T v_{in}(t) \sqrt{2} \cos\left(n \cdot \frac{2\pi}{T} \cdot t\right) dt$$

$$= \frac{1}{1 \times 10^{-9}} \left[\int_0^{.5 \text{ ns}} 5 \sqrt{2} \cos\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) dt + \int_{.5 \text{ ns}}^{1 \text{ ns}} -5 \sqrt{2} \cos\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) dt \right]$$

$$= \frac{1}{1 \times 10^{-9}} \left[\underbrace{\left[5 \sqrt{2} \cdot \frac{1 \text{ ns}}{2\pi} \sin\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) \right]_0^{.5 \text{ ns}}}_0 - \underbrace{\left[5 \sqrt{2} \cdot \frac{1 \text{ ns}}{2\pi} \sin\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) \right]_{.5 \text{ ns}}^{1 \text{ ns}}}_0 \right]$$

$$a_1 = 0$$

$$b_1 = \frac{1}{T} \int_0^T v_{in}(t) \sqrt{2} \sin\left(n \cdot \frac{2\pi}{T} \cdot t\right) dt$$

$$= \frac{1}{1 \text{ ns}} \left[\int_0^{.5 \text{ ns}} 5 \sqrt{2} \sin\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) dt + \int_{.5 \text{ ns}}^{1 \text{ ns}} -5 \sqrt{2} \sin\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) dt \right]$$

$$= \frac{1}{1 \text{ ns}} \left\{ \left[-5 \sqrt{2} \cdot \frac{1 \text{ ns}}{2\pi} \cos\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) \right]_0^{.5 \text{ ns}} + \left[5 \sqrt{2} \cdot \frac{1 \text{ ns}}{2\pi} \cos\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot t\right) \right]_{.5 \text{ ns}}^{1 \text{ ns}} \right\}$$

$$= \frac{5 \sqrt{2}}{2\pi} \left\{ \underbrace{-\cos\left(1 \cdot \frac{2\pi}{1 \text{ ns}} \cdot .5 \text{ ns}\right)}_1 + \underbrace{\cos\left(\frac{2\pi}{1 \text{ ns}} \cdot 0\right)}_1 + \underbrace{\cos\left(\frac{2\pi}{1 \text{ ns}} \cdot 1 \text{ ns}\right)}_1 - \underbrace{\cos\left(\frac{2\pi}{1 \text{ ns}} \cdot .5 \text{ ns}\right)}_1 \right\}$$

$$b_1 = \frac{10 \sqrt{2}}{\pi}$$

1.) a.) continued

$$V_{\text{Load}}(t) = \frac{10\sqrt{2}}{\pi} \cdot \sqrt{2} \sin\left(1 \cdot \frac{2\pi}{1\text{ns}} \cdot t\right)$$

$$V_{\text{Load}}(t) = \frac{20}{\pi} \sqrt{2} \sin\left(\frac{2\pi}{1\text{ns}} \cdot t\right)$$

b.) $R_L = 50 \Omega$

$$P = ? \quad P = \frac{(V_{\text{rms}})^2}{R}$$

$$V_{\text{rms}} = \frac{20}{\pi\sqrt{2}} \Rightarrow P = \frac{(20)^2}{\pi^2 2R} = \frac{400}{\pi^2 100} = \boxed{\frac{4}{\pi^2} \text{W}}$$

c.) filter passes 3GHz signals

$$3\text{GHz} \Rightarrow n=3$$

$$b_3 = ?$$

$$b_3 = \frac{1}{T} \int_0^T v_m(t) \sqrt{2} \sin\left(n \cdot \frac{2\pi}{T} \cdot t\right) dt$$

$$= \frac{1}{1\text{ns}} \left[\int_0^{0.5\text{ns}} 5\sqrt{2} \sin\left(3 \cdot \frac{2\pi}{1\text{ns}} \cdot t\right) dt + \int_{0.5\text{ns}}^{1\text{ns}} -5\sqrt{2} \sin\left(3 \cdot \frac{2\pi}{1\text{ns}} \cdot t\right) dt \right]$$

$$= \frac{1}{1\text{ns}} \left\{ \left[5\sqrt{2} \frac{1\text{ns}}{6\pi} \cos\left(\frac{6\pi}{1\text{ns}} \cdot t\right) \right]_0^{0.5\text{ns}} + \left[5\sqrt{2} \frac{1\text{ns}}{6\pi} \cos\left(\frac{6\pi}{1\text{ns}} \cdot t\right) \right]_{0.5\text{ns}}^{1\text{ns}} \right\}$$

$$= \frac{5\sqrt{2}}{6\pi} \left[\underbrace{-\cos\left(\frac{6\pi}{1\text{ns}} \cdot 0.5\text{ns}\right)}_1 + \underbrace{\cos\left(\frac{6\pi}{1\text{ns}} \cdot 0\right)}_1 + \underbrace{\cos\left(\frac{6\pi}{1\text{ns}}\right)}_1 - \underbrace{\cos\left(\frac{6\pi}{1\text{ns}} \cdot 0.5\text{ns}\right)}_1 \right]$$

$$b_3 = \frac{10\sqrt{2}}{3\pi} \Rightarrow V_{\text{Load}}(t) = \frac{10\sqrt{2}}{3\pi} \cdot \sqrt{2} \sin\left(3 \cdot \frac{2\pi}{1\text{ns}} \cdot t\right)$$

$$V_{\text{Load}}(t) = \frac{20}{3\pi} \sqrt{2} \sin\left(\frac{6\pi}{1\text{ns}} \cdot t\right)$$

$$P = \frac{400}{9\pi^2 \cdot 2 \cdot 50} = \frac{4}{9\pi^2} \text{W}$$

#####

#Problem 2

(a) Plot the following functions over one cycle , where $f = 100$ MHz.
 # Plot at least 32 points/waveform. To keep it from getting tedious,
 # please use Excel, Matlab, or some other computer program to calculate and
 # to plot.

#####

#Define Variables

f=100000000 # Frequency = 100MHz
 To=1/f #Period
 n=100 #number of points per waveform (problem says should be >32
 t=seq(from=0, to= To, by= To/n) #discrete points in time for one cycle

#Enter functions (given) and plot them

V1 = sin(2*pi*f*t)
 plot(x=t, y=V1) #Figure 1a attached

V3 = V1 + (1/3)*sin(3*2*pi*f*t)
 plot(x=t, y=V3) #Figure 1b

V5 = V3 + (1/5)*sin(5*2*pi*f*t)
 plot(x=t, y=V5) #Figure 1c

V7 = V5 + (1/7)*sin(7*2*pi*f*t)
 plot(x=t, y=V7) #Figure 1d

V9 = V7 + (1/9)*sin(9*2*pi*f*t)
 plot(x=t, y=V9) #Figure 1e


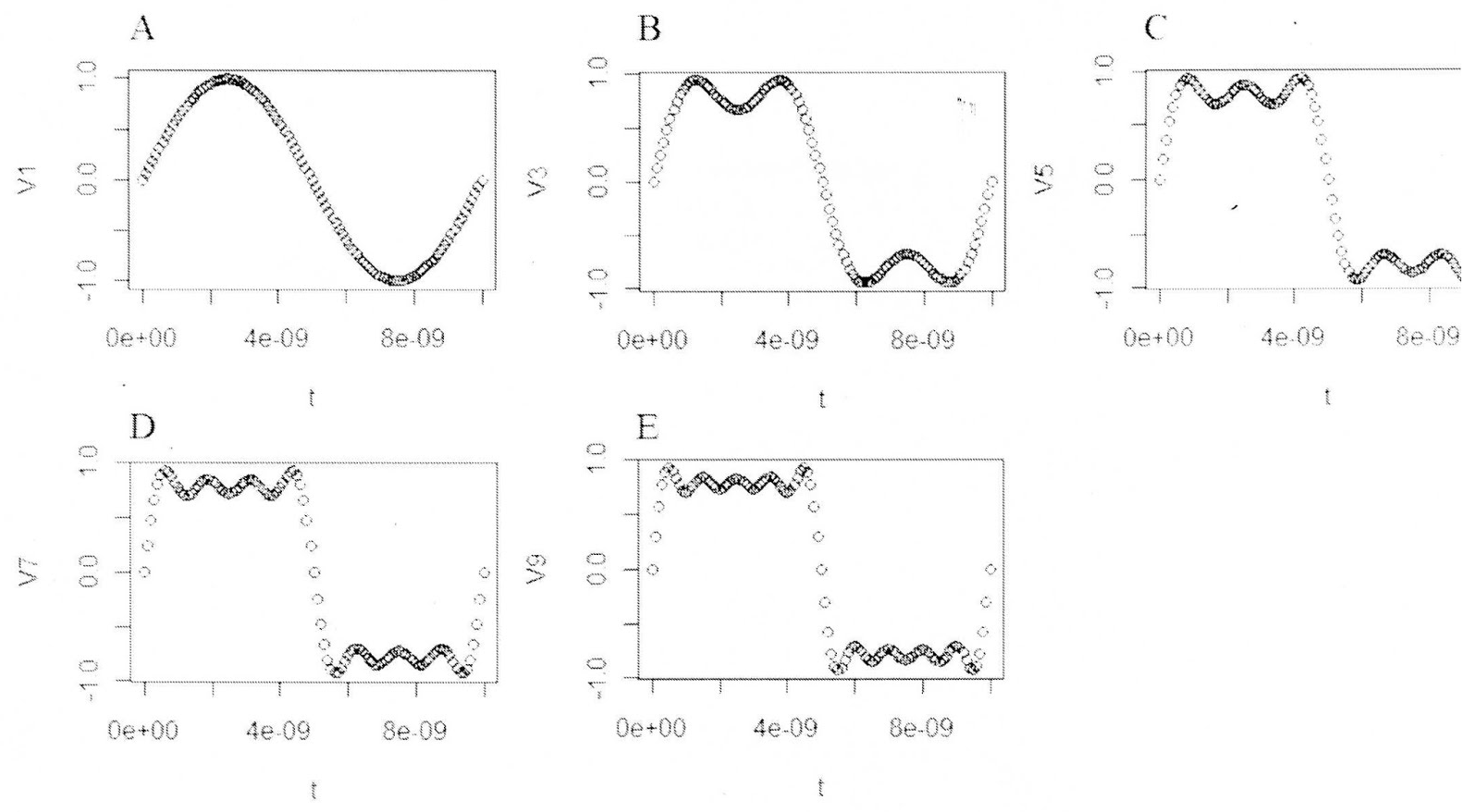


Figure 1: Plots for problem 2

```
#####
# (b)what do you think  $V_n(t)$  becomes when  $n$  is very large ?
#
# As  $n$  gets very large  $V_n(t)$  will become a square wave.
#####
```

a.)

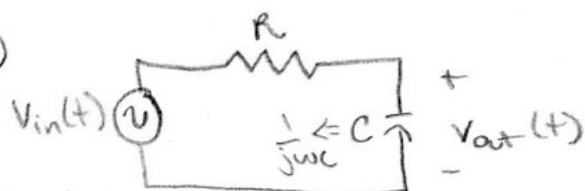

$$R = 100 \Omega$$

$$RC = 1 \text{ ns}$$

$$f = 100 \text{ MHz}$$

$$\omega_0 = 2\pi f = 2\pi \cdot 100 \text{ MHz}$$

• Find transfer function
Voltage Divider:

$$V_{out} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} \cdot V_{in} = \frac{1 \cdot V_{in}}{j\omega C \left(\frac{1}{j\omega C} + R \right)} = \frac{1}{1 + j\omega RC} V_{in}$$

$$T(j\omega) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\omega RC}$$

$$\bullet |T(j\omega)| = \left(\frac{1}{1 + j\omega RC} \right) \cdot \left(\frac{1}{1 - j\omega RC} \right) = \sqrt{\frac{1}{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (n\omega_0 RC)^2}}$$

$$\bullet \phi_T = -\tan^{-1}\left(\frac{\omega RC}{1}\right) = -\tan^{-1}\left(\frac{n\omega_0 RC}{1}\right)$$

Find Amplitude and Phase of V_{in}

$$V_{in}(t) = 1 \text{ V} \cdot \sin(2\pi f t)$$

$$|V_{in}| = 1 \text{ V}$$

$$\phi_{V_{in}} = -\pi/2$$

• Find Amplitude and phase of V_{out}

$$|V_{out}| = |V_{in}| \cdot |T(j\omega)| = 1 \text{ V} \cdot \frac{1}{\sqrt{1 + (1 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns})^2}} = 0.85 \text{ V}$$

$$\phi_{V_{out}} = \phi_{V_{in}} + \phi_T = -\pi/2 - \tan^{-1}(n\omega_0 RC) = -2.13 \text{ rad}$$

$$V_{out}(t) = 0.85 \text{ V} \cdot \cos(n\omega_0 t + \phi_{V_{out}}) \\ = 0.85 \text{ V} \cdot \cos(1 \cdot 2\pi \cdot 100 \text{ MHz} \cdot t - 2.13 \text{ rad})$$

3.) continued

$$b.) V_{in}(t) = \frac{1}{3} \cdot V \cdot \sin(3 \cdot 2\pi f t)$$

$$|V_{in}| = \frac{1}{3} \quad \phi_{vin} = -\pi/2 \quad n=3$$

$$|V_{out}| = \frac{1 \cdot V}{3} \cdot \frac{1}{1 + (3 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns})^2} = 0.156 \text{ V}$$

$$\phi_{out} = -\pi/2 - \tan^{-1}(3 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns}) = -2.65 \text{ rad}$$

$$V_{out} = 0.156 \text{ V} \cdot \cos(3 \cdot 2\pi \cdot 100 \text{ MHz} \cdot t - 2.65 \text{ rad})$$

$$c.) V_{in}(t) = \frac{1}{5} \cdot V \cdot \sin(5 \cdot 2\pi f t)$$

$$|V_{in}| = \frac{1 \cdot V}{5} \quad \phi_{vin} = -\pi/2 \quad n=5$$

$$|V_{out}| = \frac{1 \cdot V}{5} \cdot \frac{1}{1 + (5 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns})^2} = 0.061 \text{ V}$$

$$\phi_{out} = -\pi/2 - \tan^{-1}(5 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns}) = -2.83 \text{ rad}$$

$$V_{out} = 0.061 \text{ V} \cdot \cos(5 \cdot 2\pi \cdot 100 \text{ MHz} \cdot t - 2.83 \text{ rad})$$

$$d.) V_{in}(t) = \frac{1 \cdot V}{7} \sin(7 \cdot 2\pi f t)$$

$$|V_{in}| = \frac{1}{7} \text{ V} \quad \phi_{vin} = -\pi/2 \quad n=7$$

$$|V_{out}| = \frac{1 \cdot V}{7} \cdot \frac{1}{1 + (7 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns})^2} = 0.032 \text{ V}$$

$$\phi_{out} = -\pi/2 - \tan^{-1}(7 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns}) = -2.91 \text{ rad}$$

$$V_{out} = 0.032 \text{ V} \cdot \cos(7 \cdot 2\pi \cdot 100 \text{ MHz} \cdot t - 2.91 \text{ rad})$$

$$e.) V_{in}(t) = \frac{1 \cdot V}{9} \sin(9 \cdot 2\pi f t)$$

$$|V_{in}| = \frac{1}{9} \text{ V} \quad \phi_{in} = -\pi/2 \quad n=9$$

$$|V_{out}| = \frac{1 \cdot V}{9} \cdot \frac{1}{1 + (9 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns})^2} = 0.019 \text{ V}$$

$$\phi_{out} = -\pi/2 - \tan^{-1}(9 \cdot 2\pi \cdot 100 \text{ MHz} \cdot 1 \text{ ns}) = -2.97 \text{ rad}$$

$$V_{out} = 0.019 \text{ V} \cdot \cos(9 \cdot 2\pi \cdot 100 \text{ MHz} \cdot t - 2.97 \text{ rad})$$

```
#####
# Problem 3: R=100 Ohms and RC= 1nS. f=100 MHz.(a) Using Phasor analysis,
# compute note the correction ->Vout(t) if Vin (t) =1V ×sin(2pft) . <---
# (b) repeat with Vin (t) =(1/ 3)×1V ×sin(3*2pft)
# (c) repeat with Vin (t) =(1/ 5)×1V ×sin(5*2pft)
# (d) repeat with Vin (t) =(1/ 7)×1V ×sin(7*2pft)
# (e) repeat with Vin (t) =(1/ 9)×1V ×sin(9*2pft)
# use Excel, Matlab, or some other computer program to calculate and to plot
# the sum of the answers you found in parts (a-e).
#####
```

```
#Define values
```

```
f=100000000 # Frequency = 100MHz
R = 100
RC = 1e-9
Wo=2*pi*f
m=seq(from=1, to =9, by=2)
To=1/f #Period
n=100 #number of points per waveform
t=seq(from=0, to= To, by= To/n) #discrete points in time for one cycle
```

```
#Define values of amplitude and phase for Vin
```

```
AmpVin= 1/m
PhaseVin=rep(-pi/2, 5)
```

```
#Calculate amplitude and phase for Transfer function
```

```
AmpT = 1/sqrt((1+(m*Wo*RC)^2))
PhaseT = -atan(m*Wo*RC)
```

```
#Calculate amplitude and phase for Vout
```

```
AmpVout= rep(0, 5)
PhaseVout= rep(0,5)
for (i in c(1:5)){
    AmpVout[i] = AmpT[i]*AmpVin[i]
    PhaseVout[i] = PhaseT[i] + PhaseVin[i]
}#end for
```

```
#Plug in the appropriate amplitude and phase
```

```
Vout1= AmpVout[1]*cos(1*Wo*t+ PhaseVout[1])
Vout2= AmpVout[2]*cos(3*Wo*t+ PhaseVout[2])
Vout3= AmpVout[3]*cos(5*Wo*t+ PhaseVout[3])
Vout4= AmpVout[4]*cos(7*Wo*t+ PhaseVout[4])
Vout5= AmpVout[5]*cos(9*Wo*t+ PhaseVout[5])
```

```
#Add up all the parts and plot
```

```
VoutTotal= Vout1 + Vout2 +Vout3 + Vout4 + Vout5
plot (y=VoutTotal, x=t) # See figure 2
```

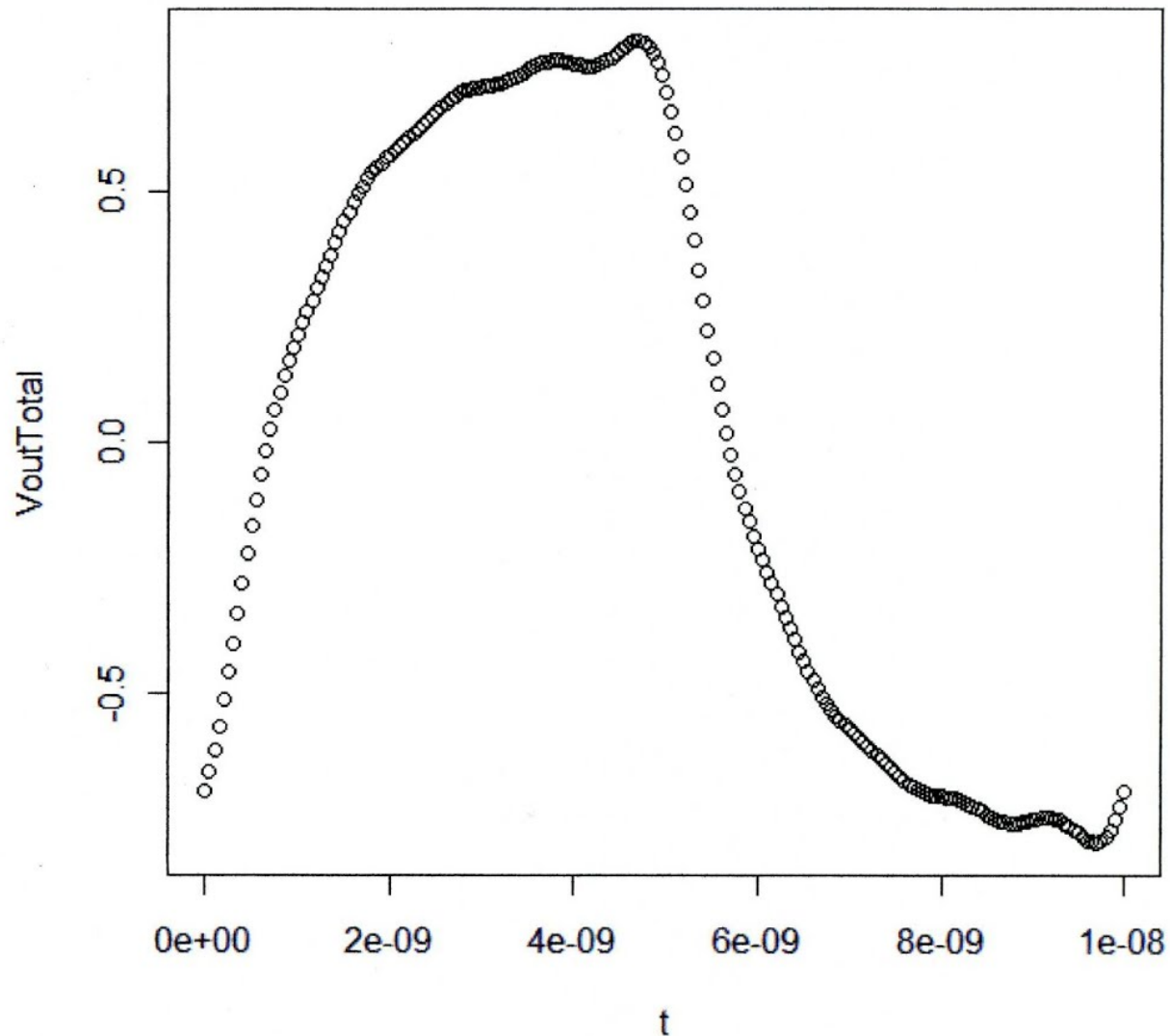


Figure 2: Plot for problem 3

Note: (a) This is an illustration of working a circuit using a square wave input, by breaking that square wave down into an input set of sine waves (Fourier series as we did in Problem 2), finding the propagation of each to the output, and then adding them up. In other words, using Fourier methods.
(b) The solution is approaching the transient solution, which is a set of charging and discharging exponentials, each with time constant $\tau=RC$.

#####

Problem 4: (a) Plot the following functions over one cycle, where $f=100$
 # MHz. Plot at least 32 points/waveform. To keep it from getting tedious,
 # please use Excel, Matlab, or some other computer program to calculate and
 # to plot.

#####

#Define Variables (same as Problem 2)

f=100000000 # Frequency = 100MHz

To=1/f #Period

n=100 #number of points per waveform (problem says should be >32

t=seq(from=0, to= To, by= To/n) #discrete points in time for one cycle

#Enter functions (given) and plot them I will call V1 VA to distinguish it
 #from problem 2

VA = sin(2*pi*f*t)

plot(x=t, y=VA) #Figure 3a attached

VB = VA - (1/2)*sin(2*2*pi*f*t)

plot(x=t, y=VB) #Figure 3b

VC = VB + (1/3)*sin(3*2*pi*f*t)

plot(x=t, y=VC) #Figure 3c

VD = VC - (1/4)*sin(4*2*pi*f*t)

plot(x=t, y=VD) #Figure 3d

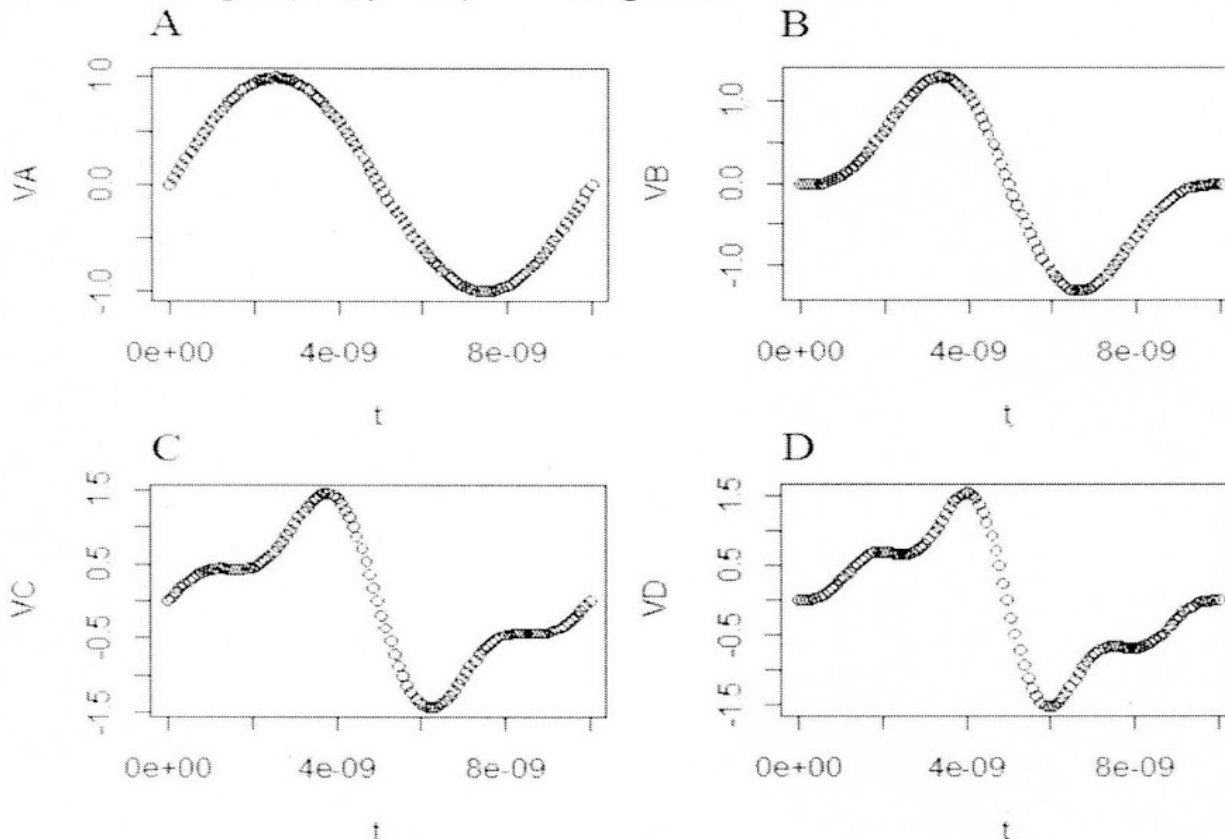


Figure 3: Plots for problem 4

#####

(b)what do you think $V_n(t)$ becomes when n is very large ?

#

As n increases this function is approaching a sawtooth wave.

#####

$$5) a.) V_{\text{sig}}(t) = a_1 V_1(t) + a_2 V_2(t) + a_3 V_3(t) + a_4 V_4(t)$$

$$\begin{aligned} a_1 &= V_{\text{sig}} \cdot V_1 = \frac{1}{T} \int_0^T V_{\text{sig}} \cdot V_1 dt \\ &= \frac{1}{4\text{ns}} \left[\int_0^{1\text{ns}} 1 \cdot 1 dt + \int_{1\text{ns}}^{2\text{ns}} -1 \cdot 1 dt + \int_{2\text{ns}}^{3\text{ns}} 1 \cdot 1 dt + \int_{3\text{ns}}^{4\text{ns}} 0 \cdot 1 dt \right] \\ &= \frac{1}{4\text{ns}} \left\{ [t]_0^{1\text{ns}} + [-t]_{1\text{ns}}^{2\text{ns}} + [t]_{2\text{ns}}^{3\text{ns}} \right\} \\ &= \frac{1}{4\text{ns}} (1\text{ns} + -2\text{ns} + 1\text{ns} + 3\text{ns} - 2\text{ns}) = \boxed{\frac{1}{4} = a_1} \end{aligned}$$

$$\begin{aligned} a_2 &= V_{\text{sig}} \cdot V_2 = \frac{1}{4} \left[\int_0^1 1 \cdot 1 dt + \int_1^2 -1 \cdot 1 dt + \int_2^3 1 \cdot -1 dt + \int_3^4 0 \cdot -1 dt \right] \\ &= \frac{1}{4} \left\{ [t]_0^1 + [-t]_1^2 + [-t]_2^3 \right\} \\ &= \frac{1}{4} [1 - 2 + 1 - 3 + 2] = \boxed{-\frac{1}{4} = a_2} \end{aligned}$$

$$\begin{aligned} a_3 &= V_{\text{sig}} \cdot V_3 = \frac{1}{4} \left[\int_0^1 1 \cdot 1 dt + \int_1^2 -1 \cdot -1 dt + \int_2^3 1 \cdot -1 dt + \int_3^4 0 \cdot 1 dt \right] \\ &= \frac{1}{4} \left\{ [t]_0^1 + [t]_1^2 + [-t]_2^3 \right\} \\ &= \frac{1}{4} [1 + 2 - 1 - 3 + 2] = \boxed{\frac{1}{4} = a_3} \end{aligned}$$

$$\begin{aligned} a_4 &= V_{\text{sig}} \cdot V_4 = \frac{1}{4} \left[\int_0^1 1 \cdot 1 dt + \int_1^2 -1 \cdot -1 dt + \int_2^3 1 \cdot 1 dt + \int_3^4 0 \cdot -1 dt \right] \\ &= \frac{1}{4} \left\{ [t]_0^1 + [t]_1^2 + [t]_2^3 \right\} = \frac{1}{4} [1 + 2 - 1 + 3 - 2] = \boxed{\frac{3}{4} = a_4} \end{aligned}$$

$$\begin{aligned} b.) V_3 \cdot V_4 &= \frac{1}{4} \left[\int_0^1 1 \cdot 1 dt + \int_1^2 -1 \cdot -1 dt + \int_2^3 -1 \cdot 1 dt + \int_3^4 1 \cdot -1 dt \right] \\ &= \frac{1}{4} \left\{ [t]_0^1 + [t]_1^2 + [-t]_2^3 + [-t]_3^4 \right\} \\ &= \frac{1}{4} [1 + 2 - 1 - 3 + 2 - 4 + 3] = 0 \checkmark \end{aligned}$$

V_3 and V_4 are orthogonal so their dot product should be